

☐ **PHYS115** ☐ **PHYS121** ☐ **PHYS123**
☐ **PHYS116** ☒ **PHYS122** ☐ **PHYS124**
Lab Cover Letter

Author (You) Trevor Swan Signature: *Trevor Swan*

I declare that this assignment is original and has not been submitted for assessment elsewhere, and acknowledge that the assessor of this assignment may, for the purpose of assessing this assignment: (1) reproduce this assignment and provide a copy to another member of faculty; and/or (2) communicate a copy of this assignment to a plagiarism checking service (which may then retain a copy of this assignment on its database for the purpose of future plagiarism checking).

Lab Partner(s) Pratham Bhashya Kerala

Date Performed 4/8/25 Date Submitted 4/15/25

Lab (such as #1: UNC) HG: LCR

TA: Samantha

GRADE (to be filled in by your TA) See your TA for detailed feedback.
 An 'x' next to a subcategory means you need to improve this aspect of your work.

Paper Subtotals (points)

- | | |
|---|---|
| <p>() General (6)</p> <p>_____ Sig. figs.</p> <p>_____ Units</p> <p>_____ Clarity of Presentation</p> <p>_____ Format</p> <p>() Abstract (4)</p> <p>_____ Quantity or principle</p> <p>_____ How measurement was made</p> <p>_____ Numerical Results</p> <p>_____ Conclusion</p> <p>() Intro & Theory (9)</p> <p>_____ Basic principle</p> <p>_____ Main equations to be used</p> <p>_____ Apparatus</p> <p>_____ What will be plotted</p> <p>_____ Fitting parameters related</p> <p>() Exp. Procedures (15)</p> <p>_____ Description</p> <p>_____ Stating and justifying uncertainties</p> <p>_____ Data Record</p> <p>_____ Quality of Lab Work</p> <p>() Analysis & Error Analysis (20)</p> <p>_____ Discussion</p> <p>_____ Equations & Calculations</p> <p>_____ Presentation inc. Graphs, Tables</p> <p>_____ Results Reported & Reasonable</p> <p>_____ Underlined items addressed</p> | <p>() Discussion & Conclusions (6)</p> <p>_____ Numerical comparison of results</p> <p>_____ Logical conclusions</p> <p>_____ Discussion of pos. errors</p> <p>_____ Suggestions to reduce errors</p> <p>() Paper Total (60 points)
 (30 points for CME or EPF)</p> <p>() Notebook (10 points)</p> <p>_____ Format (<i>proper style, following directions</i>)</p> <p>_____ Apparatus (<i>brief description of equipment, including sketches</i>)</p> <p>_____ Data (<i>including computer file names and manually recorded data</i>)</p> <p>_____ Experimental Technique (<i>describing your procedures; stating & justifying uncerts.</i>)</p> <p>_____ Analysis (<i>results and errors</i>)</p> <p>() Worksheet(s)/Fill-in-the-Blank-Report (30 points) if applicable</p> <p>() Adjustments – late submissions, improper procedures, etc. – or bonus points for exceptional work.</p> <p>() Total Grade</p> <p>Graded by _____ (TA's initial)</p> |
|---|---|

Damped and Forced Oscillators

(LCR)

Trevor Swan

Department of Physics, Case Western Reserve University
Cleveland, OH 44016-7079

4/15/25

1 Abstract

I have tested the angular frequency for forced and unforced damped LCR circuits using Lorentzian models and Origin & Logger Pro software. Using Logger Pro and various capacitor-resistor setups, I have measured the angular frequency, time constant, and damping coefficient for 6 different setups. While including numerical values for these 6 trials would be inefficient in this section, all of the data collected aligned with the theoretical values predicted. This experiment shows that measurements made in the lab are consistent with the laws of physical space. Only a handful of these values did not align within their errors, but they are minor enough that it is safe to assume repeats of the experiment would yield 'correct' results. Using Origin, a digital oscilloscope, and a function generator, I have measured the resonant angular frequency and charge stored in a capacitor in a forced LCR circuit. We found a resonant angular frequency of $\omega_R = 50907 \pm 213.6 \frac{1}{s}$, and $Q_{real} = 2.98 \pm 0.07$. This value for ω_R aligned perfectly within both its error bars and the theoretical error bars, supporting this finding. The value for Q did not, align within its error bars, and this is most likely due to nuisance variables, environmental factors, systematic errors, or even mishandled theory. While systematic errors were not heavily present in the following experiments, they did plague the final Q value, and hence we cannot claim that the theory behind Q is correct with a strong degree of certainty.

2 Introduction and Theory

2.1 Damped Oscillator

An inductor is typically a coil tightly wound into a toroid or solenoid. It can thus store energy in its magnetic field. This behavior is governed by Faraday's Law of Induction, which allows us to show that EMF's across an inductor is influenced by the current flowing through it.

In an unforced LCR circuit, the amount of charge stored in the capacitor is described by the second order linear forced differential equation

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \quad (1)$$

This is directly analogous to the mechanical equivalent of an oscillator, where the mass is replaced by the inductance L , the resistance R replaces the damping coefficient, and the spring constant term is replaced by $\frac{1}{C}$.

Using principles of differential equations, we find the solution of Equation 1 is

$$Q = Q_o e^{-(t/\tau)} \sin(\omega' t + \phi) \quad (2)$$

where

$$\omega' = \sqrt{\omega^2 - \frac{1}{\tau^2}} = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \quad (3)$$

where the parameters

1. Q_o is the charge at $t = 0$ assuming a phase angle $\phi = \frac{\pi}{2}$
2. $\tau = \frac{2L}{R}$ is the decay time for the exponential term to decrease by $1/e$.
3. $\omega^2 = \frac{1}{LC}$ where ω is given as the resonant frequency of the undamped circuit. With damping, ω' is used.

To determine the voltage across the capacitor as opposed to the charge across it, we can use the relationship $Q = CV_C$. As capacitance C is a constant, we can substitute this expression into Equation 2 and yield

$$V_R = V_o e^{-(t/\tau)} \sin(\omega' t + \phi). \quad (4)$$

To classify harmonic systems like this one, we can use the damping ratio ξ , defined

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}. \quad (5)$$

Here, if $\xi < 1$, it is underdamped, if $\xi = 1$, it is critically damped, and if $\xi > 1$, it is overdamped, as defined in the lab manual (1).

2.2 Resonant Circuit (Forced Oscillator)

An electric oscillator, like any oscillator, has its own resonant frequency given by:

$$\omega_R = \sqrt{\frac{1}{LC}}. \quad (6)$$

A periodic driving force ω from say, a function generator, will cause changes in observed voltage amplitude. If the driving force is equal to the system's resonant frequency, then the

observed amplitude will be at its maximum. If the driving force is any other value, then the system will show reduced amplitude.

In a forced LCR circuit, the amount of charge stored in the capacitor is described by the second order linear forced differential equation

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = E_m \cos \omega t \quad (7)$$

where ω is the angular frequency of the driving oscillator, given by $\omega = 2\pi f$.

Using principles of differential equations, and using the relationship $I = \frac{dQ}{dt}$, we find the solution of Equation 7 is

$$I = I_m \cos(\omega t + \phi) \quad (8)$$

where I_m is the current's amplitude and ϕ is the phase of the system. It should be noted that the current oscillates with the frequency of the function generator (driving force), and not the resonant frequency of the circuit itself.

The amplitude of the current I_m is given by the expression

$$I_m = \frac{V_m}{D} \quad (9)$$

where D is given by

$$D = \sqrt{\left(\omega L - \frac{1}{\omega C}\right)^2 + R^2} \quad (10)$$

where L is the inductance, C is the capacitance, and R is the resistance. From this expression, it is clear that I_m is at its maximum when D is at its minimum. This occurs when the driving force's frequency is equal to the resonant frequency of the system, which can be shown by

$$\omega L = \frac{1}{\omega C} \quad \rightarrow \quad \omega = \sqrt{\frac{1}{LC}} = \omega_R \quad (11)$$

Using Ohm's law, we can find that the voltage at the resonant frequency V_R is given by $V_R = I * R_R$. Here, $R = R_R$, so the distinction is not needed. We can use this relationship in combination with Equations 9 and 10 to compute the gain voltage across the resistor, which is given by the ratio V_R/V_m , where V_m is the input voltage from the driving force or function generator. The gain is thus given by

$$\frac{V_R}{V_m} = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}. \quad (12)$$

A plot of Equation 12 where $\frac{V_R}{V_m}$, or Gain, is the independent Variable and ω is the dependent variable is called a resonance curve.

The quality factor Q of a resonant circuit can be expressed both by the system's resonant frequency or qualities of the circuit as

$$Q = \frac{\omega_R L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (13)$$

3 Experimental Procedure

To construct the LCR circuits for this lab, we used a Pasco board using a $80 - 100mH$ inductor. Using an LC Meter, we measured the inductance, L , of said inductor to be $86.6 \pm 0.1mH$, as reported in Table 9. We also used 3 different capacitors in this lab, which we measured an LC Meter as well. For the $0.022\mu F$ capacitor (C_1 in Table 9), we measured a capacitance of $0.022 \pm 0.001\mu F$ using an LC Meter. For the $0.47\mu F$ capacitor (C_2 in Table 9), we measured a capacitance of $0.47 \pm 0.01\mu F$ using an LC Meter. For the $0.0047\mu F$ capacitor (C_3 in Table 9), we measured a capacitance of $0.0045 \pm 0.0001\mu F$ using an LC Meter. As noted, these values are reported in Table 9, but have been converted to their standard units (i.e $mH \rightarrow H$).

Also, we used a total of 5 different resistance measurements/values in this lab. Using a DMM, we measured the resistance of the inductor (R_{ind} in Table 8) to be $188.8 \pm 0.1\Omega$. For the 100Ω resistor (R_1 in Table 8), we measured a resistance of $99.1 \pm 0.1\Omega$. For the first 1000Ω resistor (R_2 in Table 8), we measured a resistance of $990. \pm 10.\Omega$. For the second 1000Ω resistor (R_2 in Table 8), we measured a resistance of $980. \pm 10.\Omega$. As for the 5th value, we read the marked resistance of the function generator to be 50Ω . This value does not have any associated error, as it is a property explicitly stated by the manufacturers.

For all of the above values, the error in these measurements is due to the uncertainty in the provided DMMs unless otherwise noted.

3.1 Damped Oscillator

To conduct the damped oscillator section of this experiment, we first constructed the circuit seen in Figure 1. To ensure that readings using Logger Pro were easy to make and that the trigger was consistently hit, we used both batteries as shown. For the first trial, we used a wire in place of the resistor, and capacitor C_1 . Although there is no actual resistor here, it is important to make use of the resistance of the inductor in any calculations for this and all future trials. To ensure that we set up the circuit properly, we charged the capacitor by pressing S_1 , and then briefly connected the DMM to the circuit to verify that the capacitor charges to a value near the voltage of the batteries (3V total). After verifying that the capacitor worked correctly, we were sure to disconnect the DMM from the circuit as the capacitor will discharge through it otherwise.

We then conducted 6 trials of this experiment using Logger Pro. To make Logger Pro work properly and make use of its Analysis/Fitting software, we configured a fit equation equal to Equation 4, where we fit the initial voltage $V_o = A$, the time constant $\tau = L$, the angular frequency $\omega = W$, and the phase angle $\phi = P$. This equation was inputted into Logger Pro and will be used for the remaining explanation of this experiment.

To collect data for the first trial, we con-

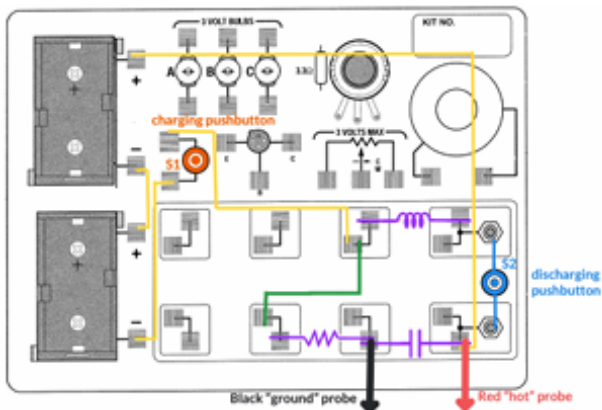


Figure 1: Experimental Apparatus of Damped Oscillator section from the LCR Manual 1

nected the logger pro probes to the red and black terminals shown in Figure 1. As we are using both batteries, we set the trigger for Logger Pro to $2.4V$ to allow for easy and automatic data collection. In this first trial, we used capacitor C_1 , and no resistor. This put the total resistance equal to just the resistance of the inductor. We then reset Logger Pro's collection by pressing the 'Collect' button, and then pressed S_1 followed by S_2 to charge and then discharge the capacitor. A plot then appeared after a brief moment, and we were able to fit a non linear curve to it as described earlier. Using the fitting software, we found values for A, L, W, P and reported them in Table 1. We then saved an image of this plot as Figure 3.

To collect data for the second trial, we replaced the capacitor with a higher rated one, C_2 . This capacitor will remain the same for the remainder of these trials. We did not change the resistance for this trial. After collecting the data and fitting a curve to it, we reported the constants in Table 2 and saved an image of this plot as Figure 4.

To collect data for the third trial, we replaced the resistor with a higher rated one, R_1 . As there is still an inductor in the circuit, the total resistance and its error were first found by adding the values in series, as reported in Equation 14. After collecting the data and fitting a curve to it, we reported the constants in Table 3 and saved an image of this plot as Figure 5.

To collect data for the fourth trial, we replaced the resistor with two higher rated ones in parallel, R_2 and R_3 . As there is still an inductor in the circuit, the total resistance and its error were first found by adding the value of the parallel resistor and the inductor's resistance in series, as reported in Equation 15. After collecting the data and fitting a curve to it, we reported the constants in Table 4 and saved an image of this plot as Figure 6.

To collect data for the fifth trial, we replaced the resistor with a higher rated one, R_2 alone. As there is still an inductor in the circuit, the total resistance and its error were first found by adding the value of the parallel resistor and the inductor's resistance in series, as reported in Equation 16. After collecting the data and fitting a curve to it, we reported the constants in Table 5 and saved an image of this plot as Figure 7.

To collect data for the fourth trial, we replaced the resistor with two higher rated ones in series, R_2 and R_3 . As there is still an inductor in the circuit, the total resistance and its error were first found by adding the value of the resistances in series as shown in Equation 17. After collecting the data and fitting a curve to it, we reported the constants in Table 6 and saved an image of this plot as Figure 8.

It should be noted that Logger Pro is an 'archaic' program and its fitting and triggering software and hardware is not state-of-the-art. It is because of this that the trigger point had to be adjusted until landing on the safe $2.4V$ limit mentioned earlier. Also, the fitting software is incredibly inconsistent, and requires multiple (sometimes 10 or more) manual attempts (continually pressing 'Try Fit') to converse on a good fit.

Using this data, we then classified the nature of the harmonic oscillators using Equation 5. We also used the properties of the circuit to calculate the theoretical ω' and τ values which will explained more in the next section.

3.2 Resonant Circuit

To conduct the resonant circuit section of this experiment, we first constructed the circuit seen in Figure 2. This circuit uses the same inductor as in the previous subsection, but uses a single $1k\Omega$ resistor (R_2) and a $0.0047\mu F$ capacitor (C_3). The circuit is driven by a function generator and the outputted signals are read by a Digital Oscilloscope (DSO). Here, the resistor, capacitor, and inductor are all wired in series with the function generator. This means that the total resistance can be found in two different ways. One way neglects the effect of the function generators resistance, which is given as $R_{gen} = 50\Omega$. The other way is to involve this resistance in series and use the total equivalent value in all calculations. In either case, the resistance of the inductor should not be ignored. The results of these calculations are discussed in the net section.

To finish setting up the function generator and DSO, we connected the Ch2 output of the function generator to the circuit and connected the DSO probes channel 1 knob. This is because the channel 2 output gives more amplitude. We then set the function generator frequency to $10kHz$ initially, and set the amplitude control to $16V_{pp}$. This voltage value will be constant throughout the experiment and can be regarded as the input voltage.

With the circuit fully set up, we then moved to acquire the data necessary to make a Gain vs. ω plot. To do this, we found the maximum amplitude shown when varying the frequency to be $10.96V$ at $8kHz$. Then, we found lower and upper bounds that were at 10% of this frequency. After finding these bounds, we took about 20 different coordinate pairs in between them to establish a resonant curve. We recorded these values into Table 7 and plotted the Gain (voltage measured divided by input voltage) against the frequency (converted to Hz for dimension homogeneity). This was plotted in Figure 9, concluding the experimental procedure for this lab.

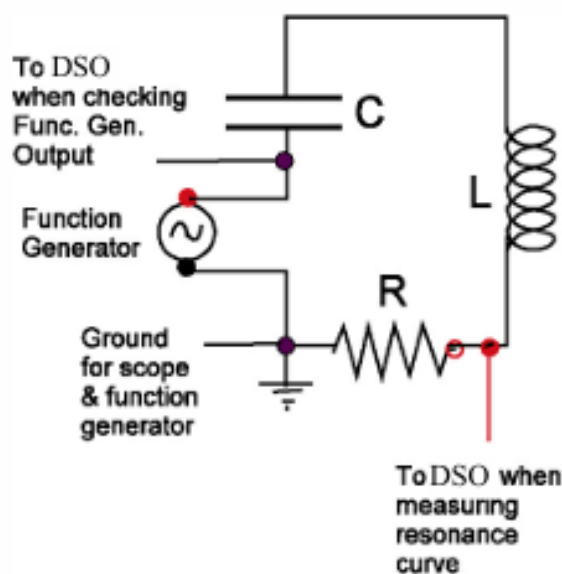


Figure 2: Experimental Apparatus of Resonant Circuit section from the LCR Manual 1

4 Results and Analysis

To assist in organization and ease of understanding, all major error analysis and calculations for the Damped Oscillator section is explained in Appendix C.2. Similarly, all of the major error analysis and calculations for the Resonant Circuit section can be found in Appendix C.3. In either case, the calculations were done using a python script, which is attached to the end of this document for your convenience in Appendix C.4.

4.1 Damped Oscillator

For the following data, we expect a severe dropoff in ω' values between Trials 1 and 2 as there is no resistor change present. We also expect there to be a smaller change between Trials 2 and 3 due to the resistance changing slightly, but capacitance being held constant. Finally, it is expected that there will be a slightly more visual drop in ω' values from Trial 3 to 4, due to the larger increase in resistance.

For trial one, we calculated $\omega' = 22884.3 \pm 521.4 \frac{1}{s}$ as shown in Equation 28. Using logger pro, we found that $\omega' = 22980 \pm 22 \frac{1}{s}$, as reported in Table 1. Comparing these two values and taking the predicted error into account, we can see that the values agree within their errors. We also calculated $\tau = 0.000917 \pm 1.2 * 10^{-6} s$ as shown in Equation 29. Using logger pro, we found that $\tau = 0.0008 \pm 2 * 10^{-5} s$. These values do not agree within their errors. Finally, we found the damping factor was $\xi = 0.048 \pm 0.001$ as shown in Equation 30. As this value is less than 1, it is clear that the system is underdamped in this state. This explains the very prominent oscillations in Figure 3.

For trial two, we calculated $\omega' = 4782.1 \pm 52.5 \frac{1}{s}$ as shown in Equation 31. Using logger pro, we found that $\omega' = 4912 \pm 5 \frac{1}{s}$, as reported in Table 2. Comparing these two values and taking the predicted error into account, we can see that the values do not agree within their errors. We also calculated $\tau = 0.000917 \pm 1.2 * 10^{-6} s$ as shown in Equation 32. This value did not change, and that is expected as we did not change resistance, and inductance is constant. Using logger pro, however, we found that $\tau = 0.0009 \pm 5 * 10^{-6} s$. These values do agree within their errors, but τ does not match the previous value, indicating some sort of systematic error or variability in the experiment. Finally, we found the damping factor was $\xi = 0.222 \pm 0.002$ as shown in Equation 33. As this value is less than 1, it is clear that the system is underdamped in this state. It should be noted that the value for ω' here aligns with the expected behavior despite not agreeing within predicted errors.

For trial three, we calculated $\omega' = 4614.5 \pm 54.4 \frac{1}{s}$ as shown in Equation 34. Using logger pro, we found that $\omega' = 4724 \pm 1 \frac{1}{s}$, as reported in Table 3. Comparing these two values and taking the predicted error into account, we can see that the values do not agree within their errors. We also calculated $\tau = 0.000602 \pm 7.5 * 10^{-7} s$ as shown in Equation 35. Using logger pro, we found that $\tau = 0.0006 \pm 5 * 10^{-7} s$. These values agree within their errors. Finally, we found the damping factor was $\xi = 0.339 \pm 0.004$ as shown in Equation 36. As this value is less than 1, it is clear that the system is underdamped in this state. This explains the oscillations in Figure 5, and also explains why the circuit reaches steady state more quickly than in the first two trials.

For trial four, we calculated $\omega' = 2929.8 \pm 89.7 \frac{1}{s}$ as shown in Equation 37. Using logger pro, we found that $\omega' = -2829 \pm 3 \frac{1}{s}$, as reported in Table 4. Comparing these two values by ignoring the negative sign and taking the predicted error into account, we can see that the values agree almost perfectly within their errors. We also calculated $\tau = 0.00025 \pm 1.3 * 10^{-6} s$ as shown in Equation 38. Using logger pro, we found that $\tau = 0.00024 \pm 1.6 * 10^{-6} s$. These values agree within their errors. Finally, we found the damping factor was $\xi = 0.802 \pm 0.009$ as shown in Equation 39. As this value is less than 1, it is mostly clear that the system is underdamped in this state. This explains the oscillations in Figure 6, and also explains why the circuit reaches steady state more quickly than in the first three trials.

For trial five, we calculated $\tau = 0.000147 \pm 1.3 * 10^{-6} s$ as shown in Equation 40. Using

logger pro, we found that $\tau = 0.000011 \pm 3s$. These values agree within their errors only because of the severe error term for the logger pro values. This term suggest an issue with the fitting model, or some other large overlooked error. Finally, we found the damping factor was $\xi = 1.39 \pm 0.02$ as shown in Equation 41. As this value is greater than 1, it is clear that the system is overdamped in this state. This explains the lack of oscillations in Figure 7.

For trial six, we calculated $\tau = 0.00008 \pm 5.3 * 10^{-7}s$ as shown in Equation 42. Using logger pro, we found that $\tau = 0.00008 \pm 0.0006s$. These values are identical and thus agree within their errors. Finally, we found the damping factor was $\xi = 2.54 \pm 0.03$ as shown in Equation 43. As this value is much greater than 1, it is very clear that the system is overdamped in this state. This explains the lack of oscillations in Figure 8, as well as the distinctly different behavior compared to the 5 other trials and their plots.

It should be clear that increasing R increases the damping constant ξ . While increasing R decreases the values for ω' due to the mathematical relationship seen in Equation 19, it does cause ξ to increase. This increase in ξ is supported by the mathematical relationship in Equation 5. As R plays a role in the differential equation as the damping coefficient (b mechanically), it makes sense that increasing R increases the value of ξ .

Decreasing C has an inverse effect on ω' due to the mathematical relationship seen in Equation 19. Decreasing C also causes ξ to decrease to a the directly proportional relationship seen in Equation 5. Decreasing C should not have an effect on the damping time constant τ , however, as C does not play a role in Equation 22. This was not the case when comparing Trials 1 and 2, though. As noted above, τ did in fact change between those trials despite L and R being held constant. This is most likely due to some experimental variability or general systematic errors between the two trials.

4.2 Resonant Circuit

We calculated the theoretical value of the resonant frequency of the circuit to be $\omega_R = 50656.5 \pm 563.6 \frac{1}{s}$ as explained in Appendix C.3. Using Origin , we plotted the Gain vs. Frequency data as shown in Figure 9 and fit Equation 12 to the data. This plot reveals a voltage amplitude $A = 0.695 \pm 0.008$. This visually aligns with the data, which is promising. The fit also revealed the Charge $Q = -2.98 \pm 0.07$. We are only concerned about the magnitude of this value, and thus I will report this value to be $Q_{real} = 2.98 \pm 0.07$. Finally, this fit revealed the resonant Frequency to be $f_R = -8102.1 \pm 34.0$. Again, the magnitude is all the matters here.

To convert the resonant frequency to the resonant angular frequency, we can multiply it and its error by 2π , according to the equation $\omega = 2\pi f$. Performing this calculation, we find that the fit shows

$$\omega_R = 50907 \pm 213.6 \frac{1}{s}.$$

Comparing this fitted/predicted value to the theory shows that the two values do in fact agree within their errors. This is most because of the large error bars on both values, but this is simply an artifact of scaling the frequency by 2π to get a useful figure. Ultimately, we can conclude that the fitted $\omega_R = 50907 \pm 213.6 \frac{1}{s}$ aligns with theory and can be reported without fear of misrepresentation.

We then calculated the charge Q in two different ways. For the first calculation, seen in Expression 51, we did not include the resistance of the function generator in the theoretical value's calculation. In this case, we found that $Q = 3.72 \pm 0.09C$. This is uncomfortably far off from the fitted value, so we then decided to account for the resistance of the function generator in the calculation. This can be seen in Expression 52 to be calculated as $Q = 3.57 \pm 0.08C$. While this number is closer to the theoretical value, it is still significantly deviated from what theory expects. This is most likely due to systematic error in our measurement techniques, or some other resistance/inductance/capacitance that we missed in our calculations. We may also find more consistent results if collecting more and more data points, though that was outside of the scope of the lab.

Ultimately, we cannot conclude that we found a suitable charge stored in the capacitor experimentally, and thus cannot confirm if theory is accurate in this scenario.

Again, all pertinent derivatives used in all error calculations can be found in the Appendix, as well as the script used to make all calculations with numerical values measured in the lab.

5 Conclusion

We have measured the angular frequencies for various damped and undamped oscillating circuits using Logger Pro, Origin, and Lorentzian Models on multiple experimental datasets/points. For our experiment concerning a damped oscillator, we found that almost all predicted values using theory aligned with the experimentally determined values. Through the use of Logger Pro's trigger and fitting software, we confidently saw alignment within errors for most values, with outliers still lying within 2-3 standard deviations of the theoretical data. While this is acceptable for drawing conclusions in this format, it should be noted that more rigorous experiments should be performed to better test the physical properties of electric oscillating circuits. Removing the effect of nuisance variables and artifacts from potentially poor fitting practices would surely increase the reliability of this experiments results. Ultimately, we found that most, almost all, of our data collected in this section of this lab agreed with the theory. This is very promising, showing that electric damped oscillators obey the laws of physics even in such an imprecise environment as an undergraduate physics lab. For our experiment concerning Resonant Circuits, we found very promising results for the resonant angular frequency of the circuit, but not so much for the charge/quality of energy Q for the experiment. We found a resonant angular frequency of $\omega_R = 50907 \pm 213.6 \frac{1}{s}$ using Origin's non-linear fitting software. This aligned perfectly within theory, despite large error bars. This is consistent with the theoretically measured $\omega_R = 50656.5 \pm 563.6 \frac{1}{s}$. In future experiments, tightening down on measurements and other causes of variability would strengthen our conclusions. For this experiment, we predicted $Q = 3.57 \pm 0.08C$ based on the used electrical components, including the resistance of the function generator. Despite taking all the correct mathematical steps to arrive at this theoretical value, it still does not align with the experimentally determined $Q_{real} = 2.98 \pm 0.07$. Ultimately, systematic errors resulted in Q not being able to be reported with my confidence or certainty.

5.1 Acknowledgments

I would like to thank Pratham Bhashyakarla, CWRU Department of Physics, for his help in obtaining the experimental data, preparing the figures, and checking my calculations.

5.2 References

1. Driscoll, D., General Physics II: E&M Lab Manual, “Damped and Forced Oscillators,” CWRU Bookstore, 2016.

A Appendix

A.1 Damped Oscillator

A (V)	L (s)	ω (1/s)	P (unitless)
-7.94 ± 0.12	$0.00078 \pm 2 * 10^{-5}$	$2.30 * 10^4 \pm 22$	-0.199 ± 0.14

Table 1: Trial data generated from Logger Pro, presented in Figure 3. This data will be referred to as 'Trial 1's data'.

A (V)	L (s)	ω (1/s)	P (unitless)
-6.17 ± 0.03	$0.00086 \pm 5 * 10^{-6}$	4912 ± 5	0.275 ± 0.004

Table 2: Trial data generated from Logger Pro, presented in Figure 4. This data will be referred to as 'Trial 2's data'.

A (V)	L (s)	ω (1/s)	P (unitless)
908.0 ± 1.3	$0.00058 \pm 5 * 10^{-7}$	4724 ± 1.3	-1.425 ± 0.005

Table 3: Trial data generated from Logger Pro, presented in Figure 5. This data will be referred to as 'Trial 3's data'.

A (V)	L (s)	ω (1/s)	P (unitless)
7.53 ± 0.07	$0.00024 \pm 2 * 10^{-6}$	-2829 ± 3	-0.337 ± 0.002

Table 4: Trial data generated from Logger Pro, presented in Figure 6. This data will be referred to as 'Trial 4's data'.

A (V)	L (s)	ω (1/s)	P (unitless)
-22.5 ± 3.0	$0.00011 \pm 1 * 10^{-6}$	$-0.0002 * 10^4 \pm 3$	0.12 ± 0.02

Table 5: Trial data generated from Logger Pro, presented in Figure 7. This data will be referred to as 'Trial 5's data'.

A (V)	L (s)	ω (1/s)	P (unitless)
-751.9 ± 9.6	0.0007 ± 0.0006	$-3.55 * 10^{-7} \pm 10$	0.0107 ± 0.0004

Table 6: Trial data generated from Logger Pro, presented in Figure 8. This data will be referred to as 'Trial 6's data'.

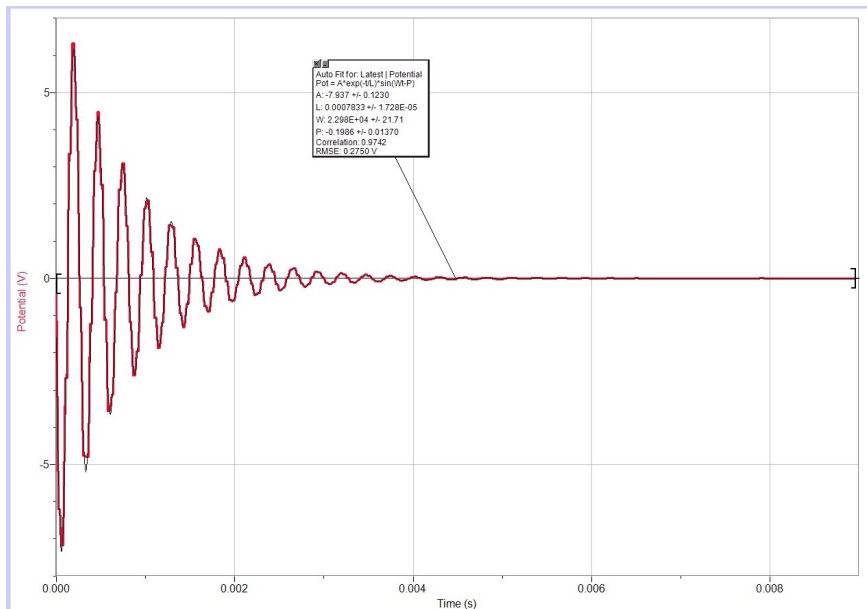


Figure 3: Damped Oscillator plot using Logger Pro of the charge stored in a capacitor inside a circuit with a $0.022 \mu\text{F}$ capacitor and no resistor. The capacitor was measured to have a capacitance of $0.022 \pm 0.001 \mu\text{F}$. There is also an $86.6 \pm 0.1\text{mH}$ inductor in the circuit.

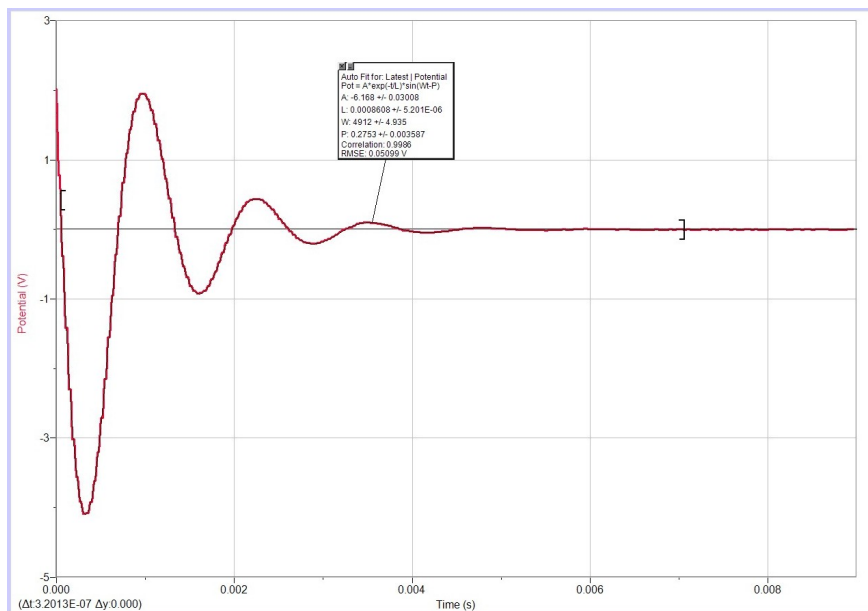


Figure 4: Damped Oscillator plot using Logger Pro of the charge stored in a capacitor inside a circuit with a $0.47 \mu\text{F}$ capacitor and no resistor. The capacitor was measured to have a capacitance of $0.47 \pm 0.01 \mu\text{F}$. There is also an $86.6 \pm 0.1\text{mH}$ inductor in the circuit.

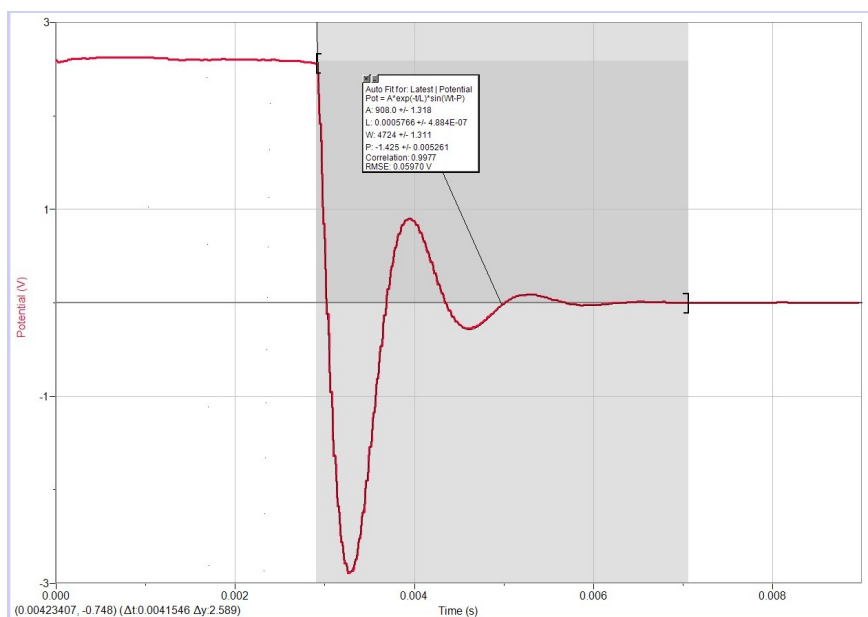


Figure 5: Damped Oscillator plot using Logger Pro of the charge stored in a capacitor inside a circuit with a $0.47 \mu\text{F}$ capacitor and a 100Ω resistor. The capacitor was measured to have a capacitance of $0.47 \pm 0.01 \mu\text{F}$, and the resistor was measured to have a resistance of $99.1 \pm 0.1\Omega$. There is also an $86.6 \pm 0.1\text{mH}$ inductor in the circuit.

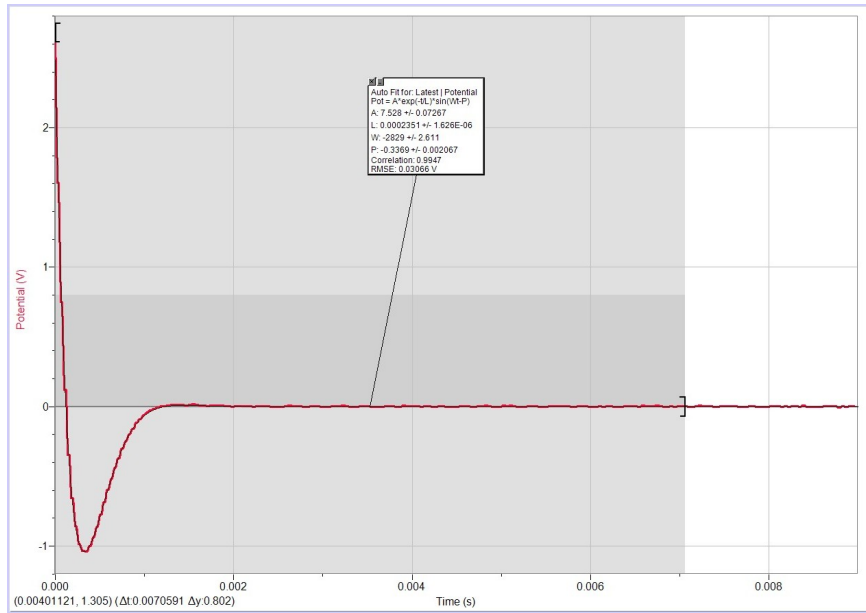


Figure 6: Damped Oscillator plot using Logger Pro of the charge stored in a capacitor inside a circuit with a $0.47 \mu\text{F}$ capacitor and a 500Ω resistor. The capacitor was measured to have a capacitance of $0.47 \pm 0.01\mu\text{F}$, and the resistor was measured to have a resistance of $492.5 \pm 0.1\Omega$. This resistor was created by combining two resistors in parallel, measuring $0.99 \pm 0.01\text{k}\Omega$ and $0.98 \pm 0.01\text{k}\Omega$, respectively. There is also an $86.6 \pm 0.1\text{mH}$ inductor in the circuit.

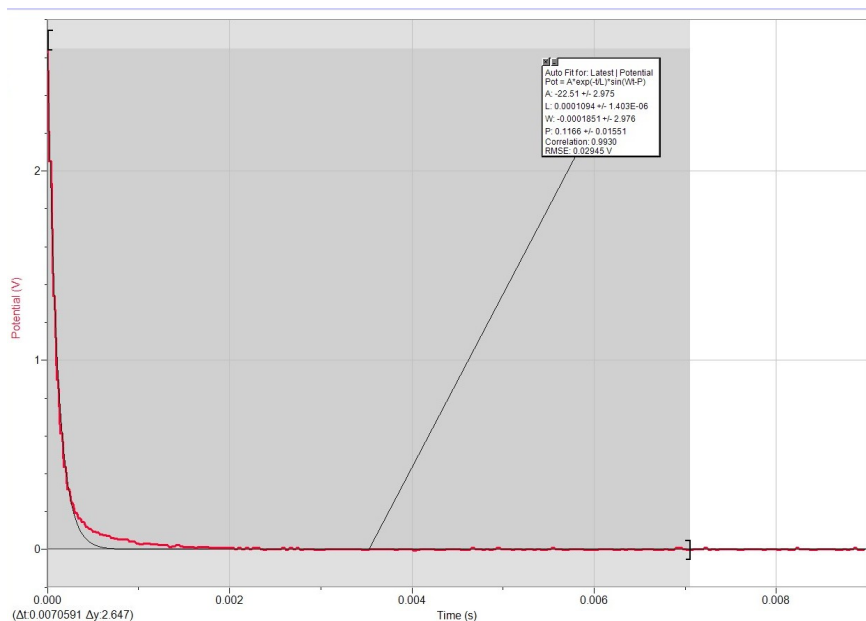


Figure 7: Damped Oscillator plot using Logger Pro of the charge stored in a capacitor inside a circuit with a $0.47 \mu\text{F}$ capacitor and a $1 \text{k}\Omega$ resistor. The capacitor was measured to have a capacitance of $0.47 \pm 0.01\mu\text{F}$, and the resistor was measured to have a resistance of $0.99 \pm 0.01\text{k}\Omega$. There is also an $86.6 \pm 0.1\text{mH}$ inductor in the circuit.

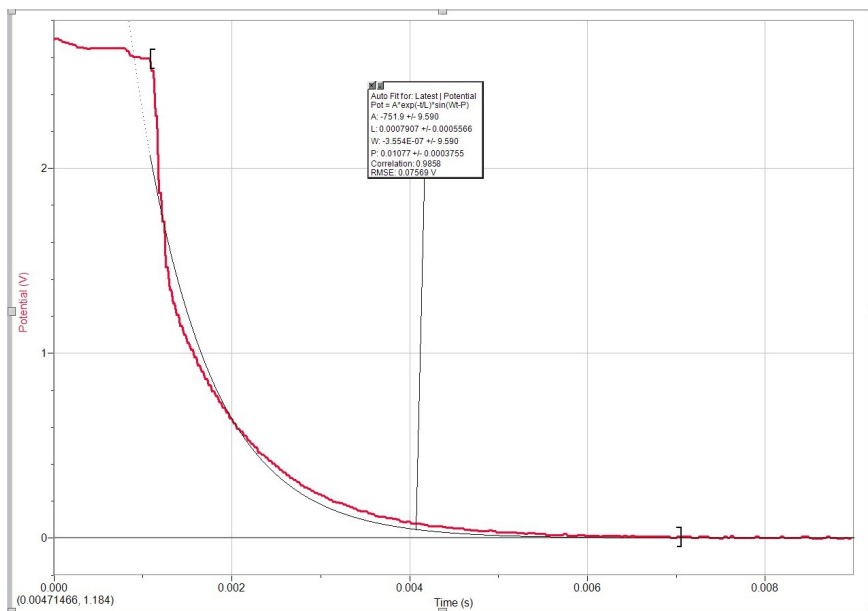


Figure 8: Damped Oscillator plot using Logger Pro of the charge stored in a capacitor inside a circuit with a $0.47 \mu\text{F}$ capacitor and a $1 \text{ k}\Omega$ resistor. The capacitor was measured to have a capacitance of $0.47 \pm 0.01 \mu\text{F}$, and the resistor was measured to have a resistance of $1.97 \pm 0.02 \text{ k}\Omega$. This resistor was created by combining two resistors in series, measuring $0.99 \pm 0.01 \text{ k}\Omega$ and $0.98 \pm 0.01 \text{ k}\Omega$, respectively. There is also an $86.6 \pm 0.1 \text{ mH}$ inductor in the circuit.

A.2 Resonant Circuit

Frequency (Hz)	Vpp (V)	Gain
2.25 ± 0.01	1.14 ± 0.02	0.07125 ± 0.00125
3.55 ± 0.01	2.02 ± 0.02	0.12625 ± 0.00125
4.85 ± 0.01	3.34 ± 0.02	0.20875 ± 0.00125
6.15 ± 0.01	5.10 ± 0.02	0.31875 ± 0.00125
7.45 ± 0.01	10.40 ± 0.02	0.65000 ± 0.00125
8.00 ± 0.01	10.96 ± 0.02	0.68500 ± 0.00125
8.75 ± 0.01	9.92 ± 0.02	0.62000 ± 0.00125
10.05 ± 0.01	6.88 ± 0.02	0.43000 ± 0.00125
11.35 ± 0.01	4.96 ± 0.02	0.31000 ± 0.00125
12.65 ± 0.01	3.92 ± 0.02	0.24500 ± 0.00125
13.95 ± 0.01	3.20 ± 0.02	0.20000 ± 0.00125
15.25 ± 0.01	2.72 ± 0.02	0.17000 ± 0.00125
16.55 ± 0.01	2.40 ± 0.02	0.15000 ± 0.00125
17.85 ± 0.01	2.16 ± 0.02	0.13500 ± 0.00125
19.15 ± 0.01	1.92 ± 0.02	0.12000 ± 0.00125
20.45 ± 0.01	1.76 ± 0.02	0.11000 ± 0.00125
21.75 ± 0.01	1.68 ± 0.02	0.10500 ± 0.00125
23.05 ± 0.01	1.52 ± 0.02	0.09500 ± 0.00125
24.35 ± 0.01	1.39 ± 0.02	0.08688 ± 0.00125
25.65 ± 0.01	1.31 ± 0.02	0.08188 ± 0.00125
26.95 ± 0.01	1.23 ± 0.02	0.07688 ± 0.00125
28.25 ± 0.01	1.18 ± 0.02	0.07375 ± 0.00125
29.00 ± 0.01	1.12 ± 0.02	0.07000 ± 0.00125

Table 7: Frequency vs. Vpp and Gain with uncertainties. Gain and its uncertainty is calculated by dividing the corresponding Vpp values by 16, the input voltage from the function generator.

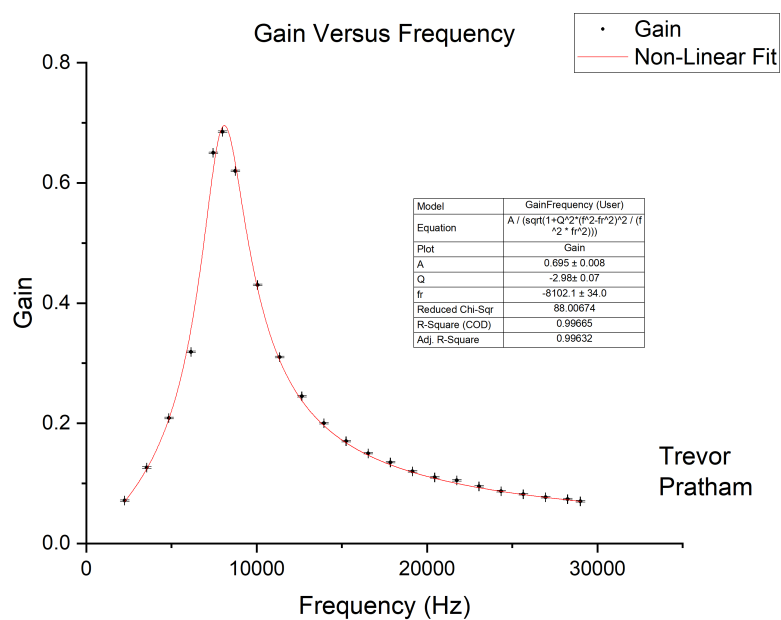


Figure 9: Plot of Gain vs. Frequency from the above table (Table 7). Non-linear fit was made using Origin, and the fitting equation along with its parameters are explained in the Theory section of this paper.

B General Data

Label	Resistance Value (R)
R_1	$99.1 \pm 0.1\Omega$
R_2	$990 \pm 10\Omega$
R_3	$980 \pm 10\Omega$
R_{ind}	$188.8 \pm 0.1\Omega$

Table 8: Resistance values and their labels used in the appendix.

Label	Measured Value (Standard Units)
L	$0.0866 \pm 0.0001H$
C_1	$2.2 * 10^{-8} \pm 1 * 10^{-9}F$
C_2	$4.8 * 10^{-7} \pm 1 * 10^{-8}F$
C_3	$4.5 * 10^{-9} \pm 1 * 10^{-10}F$

Table 9: The inductance (L) is different from the tabulated L values in tables from the previous section. It was calculated by dividing the measured value (in mH) by 1000 to get a value in H . The capacitance values were determined by dividing the measured values by 10^6 to get values in terms of F . These unit conversions are simple and easy to verbally understand, so they are omitted in this paper. These conversions were made to allow time to be represented in seconds.

C Other Calculations

C.1 General Resistance Calculations and Error

C.1.1 100 Ohm Resistor

$$\begin{aligned}
 R_{eq} &= R_1 + R_{ind} = 99.1 + 188.8 = 287.9\Omega \\
 \delta_{R_{eq}} &= \sqrt{\delta_{R_{eq}R_1}^2 + \delta_{R_{eq}R_{ind}}^2} \\
 &= \sqrt{0.1^2 + 0.1^2} = 0.1 \\
 R_{eq} &= 287.9 \pm 0.1\Omega
 \end{aligned} \tag{14}$$

C.1.2 500 Ohm Resistor

$$\begin{aligned}
R_{eq} &= \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} + R_{ind} = \left(\frac{1}{990} + \frac{1}{980} \right)^{-1} + 188.8 = 681.3\Omega \\
\delta_{R_{eq}} &= \sqrt{\delta_{R_{eq}R_2}^2 + \delta_{R_{eq}R_3}^2 + \delta_{R_{eq}R_{ind}}^2} \\
&= \sqrt{0.1^2 + 0.1^2} = 0.1 \\
\delta_{R_{eq}R_2} &= \frac{\partial}{\partial R_1} \left(\left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} + R_{ind} \right) * \delta_{R_2} = \frac{R_3^2}{(R_2 + R_3)^2} * \delta_{R_2} \\
&= \frac{980}{(990 + 980)^2} * 10 = 2.475 \\
\delta_{R_{eq}R_3} &= \frac{\partial}{\partial R_2} \left(\left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} + R_{ind} \right) * \delta_{R_3} = \frac{R_2^2}{(R_2 + R_3)^2} * \delta_{R_3} \\
&= \frac{990}{(990 + 980)^2} * 10 = 2.525 \\
\delta_{R_{eq}R_{ind}} &= \frac{\partial}{\partial R_{ind}} \left(\left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} + R_{ind} \right) * \delta_{R_{ind}} = \delta_{R_{ind}} = 0.1 \\
\delta_{R_{eq}} &= \sqrt{2.475^2 + 2.525^2 + 0.1^2} = 3.5 \\
R_{eq} &= 681.3 \pm 3.5\Omega
\end{aligned} \tag{15}$$

C.1.3 1000 Ohm Resistor

$$\begin{aligned}
R_{eq} &= R_2 + R_{ind} = 990 + 188.8 = 1178.8\Omega \\
\delta_{R_{eq}} &= \sqrt{\delta_{R_{eq}R_2}^2 + \delta_{R_{eq}R_{ind}}^2} \\
&= \sqrt{10^2 + 0.1^2} = 10 \\
R_{eq} &= 1178.8 \pm 10.0\Omega
\end{aligned} \tag{16}$$

C.1.4 2000 Ohm Resistor

$$\begin{aligned}
R_{eq} &= R_2 + R_3 + R_{ind} = 990 + 980 + 188.8 = 2158.8\Omega \\
\delta_{R_{eq}} &= \sqrt{\delta_{R_{eq}R_2}^2 + \delta_{R_{eq}R_3}^2 + \delta_{R_{eq}R_{ind}}^2} \\
&= \sqrt{10^2 + 10^2 + 0.1^2} = 14.1 \\
R_{eq} &= 2158.8 \pm 14.1\Omega
\end{aligned} \tag{17}$$

C.1.5 1000 Ohm Resistor with Function Generator

$$\begin{aligned}
 R_{eq} &= R_{1000\Omega with Inductor} + R_{FunctionGenerator} = 1178.8 + 50 = 1228.8\Omega \\
 \delta_{R_{eq}} &= \sqrt{\delta_{R_{eq}R_{1000\Omega with Inductor}}^2 + \delta_{R_{eq}R_{FunctionGenerator}}^2} \\
 &= \sqrt{10^2 + 0^2} = 10 \\
 R_{eq} &= 1228.8 \pm 10.0\Omega
 \end{aligned} \tag{18}$$

The resistance of the function generator is given on the machine to be 50Ω . As a result, it is not included with error in the calculation above.

C.2 Damped Oscillator

C.2.1 Generally Useful Expressions

The following derivation shows the equation and error for ω , the frequency. Derivatives in this section will be taken assuming $L, C, R > 0$, which is guaranteed to be true as these are physical properties that are positive by convention.

$$\omega' = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \quad (19)$$

$$\delta_{\omega'} = \sqrt{\delta_{\omega'_L}^2 + \delta_{\omega'_C}^2 + \delta_{\omega'_R}^2} \quad (20)$$

$$\delta_{\omega'_L} = \frac{\partial}{\partial L} \left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) * \delta_L = \frac{CR^2 - 2L}{2L^2 \sqrt{C(4L - CR^2)}} * \delta_L$$

$$\delta_{\omega'_C} = \frac{\partial}{\partial C} \left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) * \delta_C = \frac{1}{C^{3/2} \sqrt{4L - CR^2}} * \delta_C$$

$$\delta_{\omega'_R} = \frac{\partial}{\partial R} \left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) * \delta_R = \frac{\sqrt{C}R}{2L \sqrt{4L - CR^2}} * \delta_R$$

$$\delta_{\omega'} = \sqrt{\left(\frac{CR^2 - 2L}{2L^2 \sqrt{C(4L - CR^2)}} * \delta_L \right)^2 + \left(\frac{1}{C^{3/2} \sqrt{4L - CR^2}} * \delta_C \right)^2 + \left(\frac{\sqrt{C}R}{2L \sqrt{4L - CR^2}} * \delta_R \right)^2} \quad (21)$$

The following derivation shows the equation and error for τ , the time constant. This is the constant solved for in Logger Pro, given by L .

$$\tau = \frac{2L}{R} \quad (22)$$

$$\delta_\tau = \sqrt{\delta_{\tau_L}^2 + \delta_{\tau_R}^2} \quad (23)$$

$$\delta_{\tau_L} = \frac{\partial}{\partial L} \left(\frac{2L}{R} \right) * \delta_L = \frac{2}{R} * \delta_L$$

$$\delta_{\tau_R} = \frac{\partial}{\partial R} \left(\frac{2L}{R} \right) * \delta_R = \frac{2L}{R^2} * \delta_R$$

$$\delta_\tau = \sqrt{\left(\frac{2}{R} * \delta_L \right)^2 + \left(\frac{2L}{R^2} * \delta_R \right)^2} \quad (24)$$

The following derivation shows the equation and error for ξ , the damping coefficient.

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}} \quad (25)$$

$$\delta_\xi = \sqrt{\delta_{\xi_L}^2 + \delta_{\xi_C}^2 + \delta_{\xi_R}^2} \quad (26)$$

$$\delta_{\xi_L} = \frac{\partial}{\partial L} \left(\frac{R}{2} \sqrt{\frac{C}{L}} \right) * \delta_L = \frac{R}{4} \sqrt{\frac{C}{L^3}} * \delta_L$$

$$\delta_{\xi_C} = \frac{\partial}{\partial C} \left(\frac{R}{2} \sqrt{\frac{C}{L}} \right) * \delta_C = \frac{R}{4\sqrt{CL}} * \delta_C$$

$$\delta_{\xi_R} = \frac{\partial}{\partial R} \left(\frac{R}{2} \sqrt{\frac{C}{L}} \right) * \delta_R = \frac{1}{2} \sqrt{\frac{C}{L}} * \delta_R$$

$$\delta_\xi = \sqrt{\left(\frac{R}{4} \sqrt{\frac{C}{L^3}} * \delta_L \right)^2 + \left(\frac{R}{4\sqrt{CL}} * \delta_C \right)^2 + \left(\frac{1}{2} \sqrt{\frac{C}{L}} * \delta_R \right)^2} \quad (27)$$

C.2.2 Setup/Trial 1

Here, we will use values $L = 0.0866H$ and $\delta_L = 0.0001H$ (Table 9), C_1 from Table 9, and R_{ind} from 9. Plugging these values into equations 19, 21, 22, 24, 25, and 27 yields:

$$\omega' = 22884.3 \pm 521.4 \frac{1}{s} \quad (28)$$

$$\tau = 0.000917 \pm 1.2 * 10^{-6} s \quad (29)$$

$$\xi = 0.048 \pm 0.001 \quad (30)$$

C.2.3 Setup/Trial 2

Here, we will use values $L = 0.0866H$ and $\delta_L = 0.0001H$ (Table 9), C_2 from Table 9, and R_{ind} from 9. Plugging these values into equations 19, 21, 22, 24, 25, and 27 yields:

$$\omega' = 4782.1 \pm 52.5 \frac{1}{s} \quad (31)$$

$$\tau = 0.000917 \pm 1.2 * 10^{-6} s \quad (32)$$

$$\xi = 0.222 \pm 0.002 \quad (33)$$

C.2.4 Setup/Trial 3

Here, we will use values $L = 0.0866H$ and $\delta_L = 0.0001H$ (Table 9), C_2 from Table 9, and R_{eq} from Subsection C.1.1. Plugging these values into equations 19, 21, 22, 24, 25, and 27

yields:

$$\omega' = 4614.5 \pm 54.4 \frac{1}{s} \quad (34)$$

$$\tau = 0.000602 \pm 7.5 * 10^{-7} s \quad (35)$$

$$\xi = 0.339 \pm 0.004 \quad (36)$$

C.2.5 Setup/Trial 4

Here, we will use values $L = 0.0866H$ and $\delta_L = 0.0001H$ (Table 9), C_2 from Table 9, and R_{eq} from Subsection C.1.2. Plugging these values into equations 19, 21, 22, 24, 25, and 27 yields:

$$\omega' = 2929.8 \pm 89.7 \frac{1}{s} \quad (37)$$

$$\tau = 0.00025 \pm 1.3 * 10^{-6} s \quad (38)$$

$$\xi = 0.802 \pm 0.009 \quad (39)$$

C.2.6 Setup/Trial 5

Here, we will use values $L = 0.0866H$ and $\delta_L = 0.0001H$ (Table 9), C_2 from Table 9, and R_{eq} from Subsection C.1.3. Plugging these values into equations 22, 24, 25, and 27 yields:

$$\tau = 0.000147 \pm 1.3 * 10^{-6} s \quad (40)$$

$$\xi = 1.39 \pm 0.02 \quad (41)$$

C.2.7 Setup/Trial 6

Here, we will use values $L = 0.0866H$ and $\delta_L = 0.0001H$ (Table 9), C_2 from Table 9, and R_{eq} from Subsection C.1.4. Plugging these values into equations 22, 24, 25, and 27 yields:

$$\tau = 8.02 * 10^{-5} \pm 5.3 * 10^{-7} s \quad (42)$$

$$\xi = 2.54 \pm 0.03 \quad (43)$$

C.3 Resonant Circuit

C.3.1 Generally Useful Expressions

The following derivation shows the equation and error for ω_R , the resonant frequency.

$$\omega_R = \sqrt{\frac{1}{LC}} \quad (44)$$

$$\delta_{\omega_R} = \sqrt{\delta_{\omega_{RL}}^2 + \delta_{\omega_{RC}}^2} \quad (45)$$

$$\delta_{\omega_{RL}} = \frac{\partial}{\partial L} \left(\sqrt{\frac{1}{LC}} \right) * \delta_L = \frac{1}{2} C \left(\frac{1}{LC} \right)^{3/2} * \delta_L$$

$$\delta_{\omega_{RC}} = \frac{\partial}{\partial C} \left(\sqrt{\frac{1}{LC}} \right) * \delta_C = \frac{1}{2} L \left(\frac{1}{LC} \right)^{3/2} * \delta_C$$

$$\delta_{\omega_R} = \sqrt{\left(\frac{1}{2} C \left(\frac{1}{LC} \right)^{3/2} * \delta_L \right)^2 + \left(\frac{1}{2} L \left(\frac{1}{LC} \right)^{3/2} * \delta_C \right)^2} \quad (46)$$

Subsections C.3.2 and C.3.3 involve calculations where R changes based on involving the resistance of the function generator in the Resistance term. There is no such term in ω_R and it can therefore be calculated once. Plugging in Values of L and C_3 from Table 9 yields:

$$\omega_R = 50656.5 \pm 563.6 \frac{1}{s} \quad (47)$$

The following derivation shows the equation and error for Q , the charge through the capacitor.

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (48)$$

$$\delta_Q = \sqrt{\delta_{Q_L}^2 + \delta_{Q_C}^2 + \delta_{Q_R}^2} \quad (49)$$

$$\delta_{Q_L} = \frac{\partial}{\partial L} \left(\frac{1}{R} \sqrt{\frac{L}{C}} \right) * \delta_L = \frac{1}{2LR} \sqrt{\frac{L}{C}} * \delta_L$$

$$\delta_{Q_C} = \frac{\partial}{\partial C} \left(\frac{1}{R} \sqrt{\frac{L}{C}} \right) * \delta_C = \frac{1}{2CR} \sqrt{\frac{L}{C}} * \delta_C$$

$$\delta_{Q_R} = \frac{\partial}{\partial R} \left(\frac{1}{R} \sqrt{\frac{L}{C}} \right) * \delta_R = \frac{1}{R^2} \sqrt{\frac{L}{C}} * \delta_R$$

$$\delta_Q = \sqrt{\left(\frac{1}{2LR} \sqrt{\frac{L}{C}} * \delta_L \right)^2 + \left(\frac{1}{2CR} \sqrt{\frac{L}{C}} * \delta_C \right)^2 + \left(\frac{1}{R^2} \sqrt{\frac{L}{C}} * \delta_R \right)^2} \quad (50)$$

C.3.2 Calculations of Charge without Function Generator Resistance

Plugging in $L = 0.0866H$, $\delta_L = 0.0001H$, $C = 4.5 * 10^{-9}F$ $\delta_C = 1 * 10^{-10}F$ from Table 9 and $R = 1178.8\Omega$ and $\delta_R = 10.0\Omega$ from Equation 16 into Equations 48 and 50 yields:

$$Q = 3.72 \pm 0.09C \quad (51)$$

C.3.3 Calculations of Charge with Function Generator Resistance

Plugging in $L = 0.0866H$, $\delta_L = 0.0001H$, $C = 4.5 * 10^{-9}F$ $\delta_C = 1 * 10^{-10}F$ from Table 9 and $R = 1228.8\Omega$ and $\delta_R = 10.0\Omega$ from Equation 18 into Equations 48 and 50 yields:

$$Q = 3.57 \pm 0.08C \quad (52)$$

C.4 Python Code for Calculations

While the derivatives are included in their entirety in the above sub and sub-subsections, the plugging-in of numbers was omitted. This is to avoid issues with repetition and errors with overflowing line length. If you as the reader are interested in verifying the calculations above, you can copy-paste the following code and observe its output. At the bottom of the code, the output I got from running this code is shown in a multi-line string at the end of the file.

```
from math import sqrt, pow
import time

# trial values - R includes the resistance of the inductor!
# L, DL, C, DC, R, DR

one_1 = [0.0866, 0.0001, 2.2 * pow(10, -8), pow(10, -9), 188.8, 0.1]
two_1 = [0.0866, 0.0001, 4.8 * pow(10, -7), pow(10, -8), 188.8, 0.1]
three_1 = [0.0866, 0.0001, 4.8 * pow(10, -7), pow(10, -8), 287.9, 0.1414213562]
four_1 = [0.0866, 0.0001, 4.8 * pow(10, -7), pow(10, -8), 681.3, 3.5]
five_1 = [0.0866, 0.0001, 4.8 * pow(10, -7), pow(10, -8), 1178.8, 10.0].8, 14.1]

trials_first_part = [one_1, two_1, three_1, four_1, five_1, six_1]

# omega prime

def w(L, DL, C, DC, R, DR):
    return sqrt(1 / (L * C) - pow(R / (2 * L), 2))

def d_w_l(L, DL, C, DC, R, DR):
    numerator = C * pow(R, 2) - 2 * L
    denominator = 2 * pow(L, 2) * sqrt(C * (4 * L - C * pow(R, 2)))
    return (numerator / denominator) * DL

def d_w_c(L, DL, C, DC, R, DR):
    numerator = 1
    denominator = pow(C, 3/2) * sqrt(4 * L - C * pow(R, 2))
    return (numerator / denominator) * DC

def d_w_r(L, DL, C, DC, R, DR):
    numerator = sqrt(C) * R
    denominator = 2 * L * sqrt(4 * L - C * pow(R, 2))
    return (numerator / denominator) * DR

def d_w(d_w_l_calc, d_w_c_calc, d_w_r_calc):
    return sqrt(pow(d_w_l_calc, 2) + pow(d_w_c_calc, 2) + pow(d_w_r_calc, 2))
```

```

# tau

def t(L, DL, C, DC, R, DR):
    return (2 * L) / R

def d_t_L(L, DL, C, DC, R, DR):
    return (2 / R) * DL

def d_t_R(L, DL, C, DC, R, DR):
    return ((2 * L) / pow(R, 2)) * DR

def d_t(d_t_L_calc, d_t_R_calc):
    return sqrt(pow(d_t_L_calc, 2) + pow(d_t_R_calc, 2))

# Xi

def xi(L, DL, C, DC, R, DR):
    return (R / 2) * sqrt(C / L)

def d_xi_l(L, DL, C, DC, R, DR):
    return ((R / 4) * sqrt(C / pow(L, 3))) * DL

def d_xi_c(L, DL, C, DC, R, DR):
    return (R / (4 * sqrt(C * L))) * DC

def d_xi_r(L, DL, C, DC, R, DR):
    return (0.5 * sqrt(C / L)) * DR

def d_xi(d_xi_l_calc, d_xi_c_calc, d_xi_r_calc):
    return sqrt(pow(d_xi_l_calc, 2) + pow(d_xi_c_calc, 2) + pow(d_xi_r_calc, 2))

# runtime

def trial_calculation_1(list_input, trial_number):
    if (len(list_input) != 6): return
    if (trial_number > 4):
        return [
            t(*list_input),
            xi(*list_input)
        ]

    return [
        w(*list_input),
        t(*list_input),

```

```

        xi(*list_input)
    ]

def trial_error_calculation_1(list_input, trial_number):
    if (len(list_input) != 6): return
    if (trial_number > 4):
        return [
            d_t(d_t_R(*list_input), d_t_L(*list_input)),
            d_xi(d_xi_l(*list_input), d_xi_c(*list_input), d_xi_r(*list_input))
        ]

    return [
        d_w(d_w_l(*list_input), d_w_c(*list_input), d_w_r(*list_input)),
        d_t(d_t_R(*list_input), d_t_L(*list_input)),
        d_xi(d_xi_l(*list_input), d_xi_c(*list_input), d_xi_r(*list_input))
    ]

# trial values
# L, DL, C, DC, R, DR

one_2_no_function_generator_resistance =
[0.0866, 0.0001, 4.5 * pow(10, -9), pow(10, -10), 1178.8, 10]
two_2_yes_function_generator_resistance =
[0.0866, 0.0001, 4.5 * pow(10, -9), pow(10, -10), 1228.8, 10]

second_part_data = [one_2_no_function_generator_resistance,
two_2_yes_function_generator_resistance]

# omega sub r

def w_r(L, DL, C, DC, R, DR):
    return sqrt(1 / (L * C))

def d_w_r_l(L, DL, C, DC, R, DR):
    return (0.5 * C * pow(1 / (L * C), 3/2)) * DL

def d_w_r_c(L, DL, C, DC, R, DR):
    return (0.5 * L * pow(1 / (L * C), 3/2)) * DC

def d_w_r_tot(d_w_r_l_calc, d_w_r_c_calc):
    return sqrt(pow(d_w_r_l_calc, 2) + pow(d_w_r_c_calc, 2))

# Q

def q(L, DL, C, DC, R, DR):

```

```

    return (1 / R) * sqrt(L / C)

def d_q_l(L, DL, C, DC, R, DR):
    return ((1 / (L * R)) * sqrt(L / C)) * DL

def d_q_c(L, DL, C, DC, R, DR):
    return ((1 / (C * R)) * sqrt(L / C)) * DC

def d_q_r(L, DL, C, DC, R, DR):
    return ((1 / (R * R)) * sqrt(L / C)) * DR

def d_q(d_q_l_calc, d_q_c_calc, d_q_r_calc):
    return sqrt(pow(d_q_l_calc, 2) + pow(d_q_c_calc, 2) + pow(d_q_r_calc, 2))

def dataset_calculation_2(list_input):
    if (len(list_input) != 6): return

    return [
        q(*list_input),
        w_r(*list_input)
    ]

def dataset_error_calculation_2(list_input):
    if (len(list_input) != 6): return

    return [
        d_q(d_q_l(*list_input), d_q_c(*list_input), d_q_r(*list_input)),
        d_w_r_tot(d_w_r_l(*list_input), d_w_r_c(*list_input))
    ]

if __name__ == "__main__":
    start = time.perf_counter()

    print("Damped Oscillator Calculations:")
    for i, trial in enumerate(trials_first_part, 1):
        print(f"Trial {str(i)}:")
        result1 = trial_calculation_1(trial, i)
        result2 = trial_error_calculation_1(trial, i)
        if (len(result1) == 2):
            print(f"tau = {result1[0]} +/- {result2[0]}")
            print(f"xi = {result1[1]} +/- {result2[1]}")
            continue
        trial_w, trial_t, trial_xi = result1
        trial_dw, trial_dt, trial_dxi = result2
        print(f"omega = {trial_w} +/- {trial_dw}")

```

```

    print(f"tau = {trial_t} +/- {trial_dt}")
    print(f"xi = {trial_xi} +/- {trial_dxi}")

print("\nResonant Circuit Calculations:")
for i, dataset in enumerate(second_part_data, 1):
    print(f"Dataset {str(i)}:")
    result1 = dataset_calculation_2(dataset)
    result2 = dataset_error_calculation_2(dataset)
    dataset_q, dataset_w_r = result1
    dataset_dq, dataset_dw_r = result2
    print(f"q = {dataset_q} +/- {dataset_dq}")
    print(f"w_r = {dataset_w_r} +/- {dataset_dw_r}")

end = time.perf_counter()
elapsed_ms = (end - start) * 1000
print(f"\nCalculations took: {elapsed_ms:.4f} ms")

# output
"""
Damped Oscillator Calculations:
Trial 1:
    omega = 22884.29650922336 +/- 521.4444087809482
    tau = 0.0009173728813559321 +/- 1.1654435761341052e-06
    xi = 0.04757999463162536 +/- 0.001082005922815503
Trial 2:
    omega = 4782.124617108206 +/- 52.46760756984916
    tau = 0.0009173728813559321 +/- 1.1654435761341052e-06
    xi = 0.22224585350358758 +/- 0.0023216006329009288
Trial 3:
    omega = 4614.534046444006 +/- 54.35551481431524
    tau = 0.0006015977770059049 +/- 7.549286618055374e-07
    xi = 0.33890138360001515 +/- 0.003539558337300766
Trial 4:
    omega = 2929.8013814492842 +/- 89.74282990603875
    tau = 0.00025421987377073244 +/- 1.3385737871276907e-06
    xi = 0.8019920550423422 +/- 0.009326292051353605
Trial 5:
    tau = 0.00014692908042076688 +/- 1.2579235983829609e-06
    xi = 1.387624004820069 +/- 0.018658514492621684
Trial 6:
    tau = 8.022975727255882e-05 +/- 5.321397357121021e-07
    xi = 2.5412306596586065 +/- 0.031278778228866655

Resonant Circuit Calculations:
    Dataset 1 (without function generator resistance):

```

```
q = 3.721453201303495 +/- 0.08862414872350376
w_r = 50656.45535446374 +/- 563.6088830836692
Dataset 2 (with function generator resistance):
q = 3.5700268828910806 +/- 0.08458688494560974
w_r = 50656.45535446374 +/- 563.6088830836692
```

```
Calculations took: 0.7414 ms
"""
```