

Practice 5 Problem 1

T

p1) Two capacitor circuit

$$(a) \quad (i) \quad i_2 = \frac{dQ_2}{dt} \quad \checkmark$$

$$(ii) \quad \varepsilon - i_2 R_2 - \frac{Q_2}{C_2} = 0 \quad \checkmark$$

$$(b) \quad \text{Steady State} \Rightarrow \frac{dQ_2}{dt} = 0$$

$$\text{Now } (a-i) \Rightarrow \boxed{i_2 = 0}$$

$$(a-ii) \Rightarrow \boxed{Q_2 = C_2 \varepsilon}$$

$$(c) \quad (i) \quad i_1 = \frac{dQ_1}{dt} \quad \checkmark$$

$$i_2 = i_1 + \frac{dQ_2}{dt} \quad \checkmark$$

$$(ii) \quad \varepsilon - i_2 R_2 - i_1 R_1 - \frac{Q_1}{C_1} = 0 \quad \checkmark$$

$$\varepsilon - i_2 R_2 - \frac{Q_2}{C_2} = 0 \quad \checkmark$$

$$(c) \quad (iii) \quad t=0+ \quad \boxed{Q_1 = 0, \quad Q_2 = C_2 \varepsilon} \quad (\text{since capacitor charge doesn't jump})$$

Practice 5 Problem 1

p2) Two Capacitor Circuit

$$(C-iii) \quad \text{use } (C-i) \quad \varepsilon - i_2 R_2 - \frac{q_2}{C_2} = 0 \quad \text{sub } q_2 = C_2 \varepsilon$$

const

$$\Rightarrow -i_2 R_2 = 0 \Rightarrow \boxed{i_2 = 0}$$

$$\text{use } (C-ii) \quad \varepsilon - i_2 R_2 - i_1 R_1 - \frac{q_1}{C_1} = 0$$

$$\text{sub } q_1 = 0, i_2 = 0$$

$$\Rightarrow \boxed{i_1 = \frac{\varepsilon}{R_1}}$$

$$(iv) \quad t \rightarrow \infty \quad \frac{dq_1}{dt} = 0, \quad \frac{dq_2}{dt} = 0 \quad (\text{in steady state})$$

$$(C-i) \Rightarrow \boxed{i_1 = 0, i_2 = 0}$$

$$(C-ii) \Rightarrow \varepsilon - i_2 R_2 - \frac{q_2}{C_2} = 0 \quad \text{sub } i_2 = 0$$

$$\Rightarrow \boxed{q_2 = C_2 \varepsilon}$$

$$(C-ii) \Rightarrow \varepsilon - i_2 R_2 - i_1 R_1 - \frac{q_1}{C_1} = 0 \quad \text{sub } i_1 = i_2 = 0$$

$$\Rightarrow \boxed{q_1 = C_1 \varepsilon}$$

Practice 5 Problem 2

Phys 122 Spring 2015

Practice Probs 5

(a) Two Loop
LR circuit

(a) Initial
analysis

(i)

$$i_1, i_2$$

$$(ii), \quad \epsilon_1 - i_1 R_1 - L \frac{di_1}{dt} = 0$$

(iii) Set $\frac{di_1}{dt} = 0$ (steady state)

$$\Rightarrow i_1 = \frac{\epsilon_1}{R_1}$$

(b) Kirchhoff
analysis

(i)

$$i_1 = i_2$$

$$(ii), \quad \epsilon_2 - i_2 R_2 - L \frac{di_2}{dt} = 0$$

$t \rightarrow 0^+$ (c)
behavior

$$(i) \quad i = \frac{\epsilon_1}{R_1}$$

(current in an inductor
cannot change)

from (a-iii), abruptly)

(iii) Set $i = \frac{\epsilon_1}{R_1}$ in part (b-ii)

$$\Rightarrow \epsilon_2 - \epsilon_1 \frac{R_2}{R_1} - L \frac{di}{dt} = 0$$

$$\Rightarrow \frac{di}{dt} = \left(\epsilon_2 - \epsilon_1 \frac{R_2}{R_1} \right) \frac{L}{L}$$

Practice 5 Problem 2

p4)

Phys 122 Spring 2015

Practice probs 5

(2) Two loop
LR

(d)

$t \rightarrow \infty$

behavior

Set $\frac{di}{dt} = 0$ in part (b-ii)

$$\Rightarrow \varepsilon_2 - i R_L = 0$$

\Rightarrow

$$i = \frac{\varepsilon_2}{R_L}$$

Practice 5 Problem 3

p1) Physics 122 Series LCR Circuit

(a)

$$(i) \quad Z_1 = i\omega L$$

$$Z_2 = -\frac{i}{\omega C}$$

$$Z_3 = R$$

(b)

$$\epsilon_0 - \tilde{I}(Z_1 + Z_2 + Z_3) = 0 \quad (\text{Kirchhoff loop rule})$$

$$\Rightarrow \tilde{I} = \frac{\epsilon_0}{Z_1 + Z_2 + Z_3} =$$

$$\frac{\epsilon_0}{R + i(\omega L - \frac{1}{\omega C})}$$

(c)

$$\tilde{I} = \frac{\epsilon_0}{R + i(\omega L - \frac{1}{\omega C})} \cdot \frac{[R - i(\omega L - \frac{1}{\omega C})]}{[R - i(\omega L - \frac{1}{\omega C})]}$$

$$= \frac{\epsilon_0}{R^2 + (\omega L - \frac{1}{\omega C})^2} [R - i(\omega L - \frac{1}{\omega C})]$$

$$\Rightarrow R < \tilde{I} = \frac{\epsilon_0 R}{[R^2 + (\omega L - \frac{1}{\omega C})^2]}$$

$$gm \tilde{I} = -\frac{\epsilon_0 (R - i(\omega L - \frac{1}{\omega C}))}{[R^2 + (\omega L - \frac{1}{\omega C})^2]}$$

Practice 5 Problem 3

p2) Physics 122 Series LCR Circuit

(d)

$$|\tilde{I}| = \frac{|\epsilon_0|}{R + i(\omega L - \frac{1}{\omega C})} = \boxed{\frac{\epsilon_0}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}}}$$

[we have used 15c rule]

$$\left| \frac{z_1}{z_2} \right| = \frac{|z_1|}{|z_2|} \text{ for } z_1 \text{ & } z_2 \text{ complex numbers}$$

Also if $\epsilon = x + iy$ then $|z| = \sqrt{x^2 + y^2}$

$$\phi = \tan^{-1} \left(\frac{\text{Im } \tilde{I}}{\text{Re } \tilde{I}} \right)$$

$$\Rightarrow \phi = \tan^{-1} \left[\left(\frac{\frac{L}{C\omega} - \omega L}{R} \right) \right]$$

(e)

$$|\tilde{I}|^2 = \frac{\epsilon_0^2}{R^2 + (\frac{1}{\omega C} - \omega L)^2}$$

$|\tilde{I}|^2$ is max when denominator is minimum

R^2 is fixed so denominator is min

when $(\frac{1}{\omega C} - \omega L)^2$ is minimum

Practice 5 Problem 3

73) Physics 122 Series LCR Circuit


(e)
cont'd

Since $\left(\frac{1}{\omega} - L\omega\right)^2$ is not negative its minimum value is zero

$$\left(\frac{1}{\omega} - L\omega\right)^2 = 0 \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

Also $|\tilde{I}|^2 \rightarrow 0$ as $\omega \rightarrow 0$

& $|\tilde{I}|^2 \rightarrow 0$ as $\omega \rightarrow \infty$

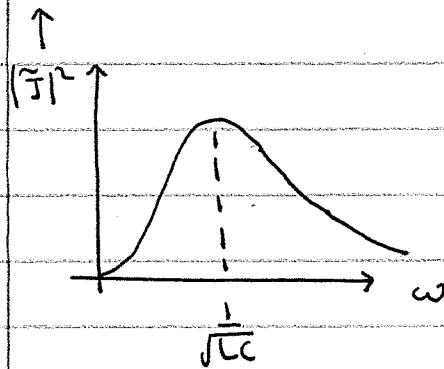

$$(f) I = \operatorname{Re} (\tilde{I} e^{i\omega t})$$

$$= \operatorname{Re} (\tilde{I} e^{i\phi} e^{i\omega t})$$

$$= \operatorname{Re} [|\tilde{I}| e^{i(\omega t + \phi)}]$$

using Euler's
formula

$$\Rightarrow I = |\tilde{I}| \cos(\omega t + \phi)$$

$$e^{i\theta} = \cos\theta + i\sin\theta$$

Practice 5 Problem 4

(a)

Two loop AC circuit

(g)

$$\boxed{Z_1 = i\omega L}, \quad \boxed{Z_2 = -\frac{i}{\omega C}}, \quad \boxed{Z_3 = R}$$

(b)

$$(i) \quad \epsilon_0 - \tilde{J}_1 Z_1 - \tilde{J}_2 Z_2 = 0$$

$$(ii) \quad \tilde{J}_2 Z_2 - \tilde{J}_3 Z_3 = 0$$

$$(iii) \quad \tilde{J}_1 = \tilde{J}_2 + \tilde{J}_3$$

(c)

$$(b - ii) \Rightarrow \tilde{J}_3 = \tilde{J}_2 \frac{Z_2}{Z_3}$$

$$\text{Sub into } (b - iii) \Rightarrow \tilde{J}_1 = \tilde{J}_2 \left(1 + \frac{Z_2}{Z_3} \right)$$

$$\Rightarrow \tilde{J}_2 = \left(\frac{Z_3}{Z_2 + Z_3} \right) \tilde{J}_1$$

$$\text{Sub into } (b - i) \Rightarrow \epsilon_0 - \tilde{J}_1 Z_1 - \frac{Z_2 Z_3}{Z_2 + Z_3} \tilde{J}_1 = 0$$

$$\Rightarrow \tilde{J}_1 = \frac{\epsilon_0}{\left(Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} \right)} \quad \text{Note } \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{1}{\frac{1}{Z_2} + \frac{1}{Z_3}}$$

$$\Rightarrow \tilde{J}_1 = \frac{\epsilon_0}{i\omega L + \frac{1}{(\frac{1}{R} + i\omega C)}} = \frac{1}{i\omega C + \frac{1}{R}}$$

Practice 5 Problem 5

p) Loop in field

(a) $\phi = 0$ for $\xi < 0$

$$= B_a \xi \quad \text{for } 0 < \xi < b$$

$$= B_a b \quad \text{for } \xi > b$$

(b) (i) $\epsilon = -\frac{d\phi}{dt} = 0$ for $\xi < 0$

$$= B_a \frac{d\xi}{dt} = B_a v \quad \text{for } 0 < \xi < b$$

$$= 0 \quad \text{for } \xi > b$$

(ii) Magnetic forces

\vec{B} is fixed so no induced electric fields

(c) (i) $i = \frac{\epsilon}{R} = \boxed{\frac{B_a v}{R}}$ (Ohm's law)

(ii) clockwise (Then induced field will point
into the page and try to
oppose the increase in external
flux through the moving loop)

(iii) $P_{\text{Joule}} = i^2 R = \boxed{\frac{B_a^2 g^2 v^2}{R}}$

Practice 5 Problem 5

p2) Loop in field

(d) (i) . use $\vec{F} = i\vec{l} \times \vec{B}$

For top segment $\vec{l} = a\hat{i}$

$$\vec{B} = \hat{k}B$$

$$i = \frac{Ba}{R}\hat{v}$$

$$\Rightarrow \boxed{\vec{F} = -\frac{B^2 a^2 v}{R} \hat{j}} \quad \text{since } \hat{i} \times \hat{k} = -\hat{j}$$

(ii) $P_{exr} = \vec{F}_{exr} \cdot \vec{v}$ ↓ velocity of loop

$$= \underbrace{\left(\frac{B^2 a^2 v}{R} \hat{j} \right)}_{\vec{F}_{exr}} \cdot (v\hat{j})$$

$$= \boxed{\frac{B^2 a^2 v^2}{R}}$$

Practice 5 Problem 6

p14, Phys 122 Spring 2014

Practice Probs 5

(5) Generator (a) $\phi = (\hat{n} \cdot \vec{B}) A$

$$\hat{n} \cdot \vec{B} = B \cos(\omega t)$$

↑ angle between \vec{B} & \hat{n}
magnitude of \vec{B}

$$\text{magnitude of } \hat{n} = 1$$

$$A = a^2$$

thus

$$\phi = a^2 B \cos(\omega t)$$

(b)

$$\varepsilon = -\frac{d\phi}{dt} = a^2 B \omega \sin \omega t$$

By Faraday's flux rule.