

**PHYS115 PHYS121 PHYS123
PHYS116 PHYS122 PHYS124
Lab Cover Letter**

Author (You) Trevor Swan

Signature: 

I declare that this assignment is original and has not been submitted for assessment elsewhere, and acknowledge that the assessor of this assignment may, for the purpose of assessing this assignment: (1) reproduce this assignment and provide a copy to another member of faculty; and/or (2) communicate a copy of this assignment to a plagiarism checking service (which may then retain a copy of this assignment on its database for the purpose of future plagiarism checking).

Lab Partner(s) Pratham Bhashya Kurla

Date Performed 1/21/25

Date Submitted 1/27/25

Lab (such as #1: UNC) #1: DCC12

TA: Samantha

GRADE (to be filled in by your TA) See your TA for detailed feedback.

An 'x' next to a subcategory means you need to improve this aspect of your work.

Paper Subtotals (points)

() **General (6)**

____ Sig. figs.
 ____ Units
 ____ Clarity of Presentation
 ____ Format

() **Abstract (4)**

____ Quantity or principle
 ____ How measurement was made
 ____ Numerical Results
 ____ Conclusion

() **Intro & Theory (9)**

____ Basic principle
 ____ Main equations to be used
 ____ Apparatus
 ____ What will be plotted
 ____ Fitting parameters related

() **Exp. Procedures (15)**

____ Description
 ____ Stating and justifying uncertainties
 ____ Data Record
 ____ Quality of Lab Work

() **Analysis & Error Analysis (20)**

____ Discussion
 ____ Equations & Calculations
 ____ Presentation inc. Graphs, Tables
 ____ Results Reported & Reasonable
 ____ Underlined items addressed

() **Discussion & Conclusions (6)**

____ Numerical comparison of results
 ____ Logical conclusions
 ____ Discussion of pos. errors
 ____ Suggestions to reduce errors

() **Paper Total (60 points)
 (30 points for CME or EPF)**

() **Notebook (10 points)**

____ Format (*proper style, following directions*)
 ____ Apparatus (*brief description of equipment, including sketches*)
 ____ Data (*including computer file names and manually recorded data*)
 ____ Experimental Technique (*describing your procedures; stating & justifying uncerts.*)
 ____ Analysis (*results and errors*)

() **Worksheet(s)/Fill-in-the-Blank-Report (30 points) if applicable**

() **Adjustments** – late submissions, improper procedures, etc. – or bonus points for exceptional work.

() **Total Grade**

Graded by _____ (TA's initial)

DC-CIR Worksheet

Your Name: Trevor Sun Signature: Trevor Sun

Lab partner(s): Pratham Bhashya Kurla

Course & Section: 122 & 118-B Station # 118-B Date: 1/26/25

Section D: Ohm's Law

- DMM reading for the resistor: $99.0 \pm 0.1 \Omega$
- List your data for minimum and maximum current, with error estimates. Don't forget units. Also, staple to this worksheet a copy of your plot, including the linear fit.

$I_{\min}: 0.0202 \pm 0.0001$ A $V: 1.99 \pm 0.01$ ✓
units
 $I_{\max}: 0.0244 \pm 0.0001$ A $V: 2.40 \pm 0.01$ ✓

- List your linear fit parameters, with error estimates from Origin. Also attached

SLOPE: 98.0 ± 1.1 Ω INTERCEPT: 0.013 ± 0.024 ✓

- Comment on the comparison of the DMM value and Origin fit. (Use additional sheets if necessary.)
 The measured value for our resistor using the DMM was $99.0 \pm 0.01 \Omega$.
 The slope determined using origin was $98.0 \pm 1.1 \Omega$. With this in mind, we can claim that our DMM was functioning properly as the values agree within their errors. Specifically $99.0 \in (97.9, 99.1)$.

Section E.1: Series Resistors

- Enter below the data (with error estimates) for series resistors.

Resistor #	Resistance (ohms)	Theoretical Sum (ohms)	Voltage (V)	Current (A or mA) (circle one)	Experimental Sum (ohms)
1	99.0 ± 0.1	99.0 ± 0.1	2.55 ± 0.01	0.0258 ± 0.0001	98.8 ± 0.5
2	99.2 ± 0.1	198.2 ± 0.1	2.64 ± 0.01	0.0133 ± 0.0001	199 ± 2
3	980 ± 10	1178.2 ± 10.0	2.7 ± 0.1	0.0023 ± 0.0001	1217 ± 15
4	98.4 ± 0.1	1226.6 ± 10.0	2.7 ± 0.1	0.0022 ± 0.0001	1227 ± 58

- Attach a sheet that describes in detail how you found the errors in each entry for two resistors in series. This should include errors in any raw data you took as well as error propagation through any equations that you used (see App. V of the lab manual).
- Compare the theory to the experiment. (Use additional sheets if necessary.)

All of our measurements, except the third, are almost perfectly in line with the theoretical sums. Excluding R_3 , all theoretical results are well within the errors of the experimental results, indicating

strong correlation and support for resistors in series. *Ultimately, ohm's law holds for resistors in series.

*The large discrepancy in R_3 is most likely due to improper circuit design that was fixed for R_4 . This would result in different I, V, and R values!

Section E.2: Parallel Resistors

8. Enter below the data from your table of part E.2 for parallel resistors

Resistor #	Resistance (ohms)	Theoretical Sum (ohms)	Voltage (V)	Current (A or mA) (circle one)	Experimental Sum (ohms)
1	99.0 ± 0.1	99.0 ± 0.1	2.56 ± 0.01	0.0260 ± 0.0001	48.46 ± 0.54
2	99.2 ± 0.1	49.55 ± 0.04	2.40 ± 0.01	0.0240 ± 0.0001	49.38 ± 0.59
3	980 ± 10	47.17 ± 0.04	2.5 ± 0.1	0.0511 ± 0.0001	48.92 ± 1.96
4	48.4 ± 0.1	23.89 ± 0.03	2.3 ± 0.1	0.0908 ± 0.0001	25.33 ± 1.10

9. Attach a sheet that describes in detail how you found the errors in each entry for 2 resistors in parallel.

10. Compare the theory to the experiment. (Use additional sheets if necessary.)

All theoretical sums except for R_4 , agree with their corresponding experimental sums. While R_1 is barely in the margin of error, R_2 and R_3 both are well within their experimental error values. Similar to my comment on the discrepancy found in our series experiment, this is likely due to issues with our circuit setup. Due to the number of resistors we placed between the connections, I would not be surprised if our final measurements off due to some sort of interference. Though this resistor doesn't agree with ohm's law, it is close enough, and the other data points support the inverse sum relationship between resistance (resistor in parallel). It is for this reason that I'd argue ohm's law is valid for resistors in parallel!

Sections F & G. Where Ohm's Law Fails & Power Limits

11. What resistance did you measure with the DMM? $1.4 \pm 0.1 \Omega$

12. Attach your Origin plot of R vs. I .

13. Comment on Ohm's Law as it applies to the incandescent bulb and compare the DMM reading to the data in your plot: (Use additional sheets if necessary.)

Ohm's Law fails with the bulb as it requires constant resistance for the linear $V=IR$ to hold. With this model, we got a resistance value of $\sim 1.4 \Omega$ from the first few data points, but the resistance increased as the current increased. The increase in resistance was clearly non-linear and actually more sigmoidal or quadratic. This is much different than the predicted (constant) resistance of $R = 1.4 \pm 0.1 \Omega$. This can be explained by the fact that bulbs contain a filament whose resistance increases as the temperature of it increases. As the increased current heats the filament, resistance increases, violating the key assumption of Ohm's Law.

14. What is the maximum rated voltage for a 100Ω , $\frac{1}{4}$ -watt resistor $5 \checkmark$ $P = \frac{V^2}{R} \Rightarrow V = \sqrt{RP} = \sqrt{100 \cdot 0.25}$

15. What is your personal resistance? $50.4 \text{ k}\Omega$

16. What voltage across your hands would result in a power that could destroy a 100Ω , $\frac{1}{4}$ -watt resistor?

2520 V

$$P = I^2 R \Rightarrow I = \sqrt{\frac{P}{R}} = \sqrt{\frac{0.25 \text{ W}}{100 \Omega}} = 0.05 \text{ A}$$

$$\Rightarrow V = 0.05 \text{ A} \cdot 50.4 \text{ k}\Omega = 2520 \text{ V}$$

GRADE: _____
(out of 30 points)

GRADED BY _____
(TA's initials)

Series Resistors - Error Propagation

Measured Resistors

$$R_1 = 99.0 \pm 0.1$$

$$R_2 = 99.2 \pm 0.1$$

$$R_3 = 980 \pm 10$$

$$R_4 = 48.4 \pm 0.1$$

Theoretical Sum's Error calculation

$$\delta_{tot1} = 0.1$$

$$\delta_{tot2} = \sqrt{\delta_{R_1} + \delta_{R_2}} = \sqrt{0.1^2 + 0.1^2} = 0.14 = 0.1$$

$$\delta_{tot3} = \sqrt{\delta_{R_1} + \delta_{R_2} + \delta_{R_3}} = \sqrt{0.1^2 + 0.1^2 + 10^2} = 10.0$$

$$\delta_{tot4} = \sqrt{\delta_{R_1} + \delta_{R_2} + \delta_{R_3} + \delta_{R_4}} = \sqrt{0.1^2 + 0.1^2 + 10^2 + 0.1^2} = 10.0$$

Experimental Sum's Error

$$R_{equiv} = \frac{V}{I} \quad (\text{refer to as } R)$$

$$\Rightarrow \delta_R = \sqrt{\delta_{R_V}^2 + \delta_{R_I}^2} \quad \delta_R = \sqrt{\left(\frac{\delta_V}{I}\right)^2 + \left(\frac{\delta_I \cdot V}{I^2}\right)^2}$$

$$\delta_{R_V} = \left| \frac{\delta R}{\delta V} \right| \cdot \delta_V = \frac{\delta_V}{I}, \quad \delta_{R_I} = \left| \frac{\delta R}{\delta I} \right| \cdot \delta_I = \left| \frac{-V}{I^2} \right| \cdot \delta_I = \frac{\delta_I \cdot V}{I^2}$$

Original Data

$$R_1: 2.55 \pm 0.01$$

$$R_2: 2.64 \pm 0.01$$

$$R_3: 2.7 \pm 0.1$$

$$R_4: 2.7 \pm 0.1$$

$$0.0258 \pm 0.0001$$

$$0.0133 \pm 0.0001$$

$$0.0023 \pm 0.0001$$

$$0.0022 \pm 0.0001$$

$V \pm \delta_V$

$\{V\}$

$I \pm \delta_I$

$\{I\}$

→ Calculations

$$\delta_{R_1} = \sqrt{\left(\frac{0.01}{0.0258}\right)^2 + \left(\frac{0.0001 \cdot 2.55}{0.0258^2}\right)^2} = 0.54497 = 0.5$$

$$\delta_{R_2} = \sqrt{\left(\frac{0.01}{0.0133}\right)^2 + \left(\frac{0.0001 \cdot 2.64}{0.0133^2}\right)^2} = 1.6711 = 2$$

$$\delta_{R_3} = \sqrt{\left(\frac{0.1}{0.0023}\right)^2 + \left(\frac{0.0001 \cdot 2.7}{0.0023^2}\right)^2} = 15.2245 = 15$$

$$\delta_{R_4} = \sqrt{\left(\frac{0.1}{0.0022}\right)^2 + \left(\frac{0.0001 \cdot 2.7}{0.0022^2}\right)^2} = 55.9700 = 58$$

Parallel Resistors - Error Propagation

Measured Resistors

$$R_1 = 99.0 \pm 0.1$$

$$R_2 = 99.2 \pm 0.1$$

$$R_3 = 980 \pm 10$$

$$R_4 = 98.4 \pm 0.1$$

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$\Rightarrow R_{total} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1}$$

$$\delta_{R_{total}} = \sqrt{\left| \frac{\partial R}{\partial R_1} \right| \delta_{R_1}^2 + \left| \frac{\partial R}{\partial R_2} \right| \delta_{R_2}^2 + \left| \frac{\partial R}{\partial R_3} \right| \delta_{R_3}^2 + \left| \frac{\partial R}{\partial R_4} \right| \delta_{R_4}^2}$$

$$S_{tot1} = 0.1 \rightarrow S_{tot1} \quad S_{tot2} \quad S_{tot3} \quad S_{tot4}$$

$$\delta_{tot2} = \sqrt{\left(\frac{R_2^2}{(R_1 + R_2)^2} \cdot \delta_{R_1} \right)^2 + \left(\frac{R_1^2}{(R_1 + R_2)^2} \cdot \delta_{R_2} \right)^2} = 0.0354$$

$$\delta_{tot3} = \sqrt{\left(\frac{R_2^2 R_3^2}{(R_1(R_2 + R_3) + R_2 R_3)^2} \cdot \delta_{R_1} \right)^2 + \left(\frac{R_1^2 R_3^2}{(R_1(R_2 + R_3) + R_2 R_3)^2} \cdot \delta_{R_2} \right)^2 + \left(\frac{R_1^2 R_2^2}{(R_1(R_2 + R_3) + R_2 R_3)^2} \cdot \delta_{R_3} \right)^2}$$

$$= 0.0395$$

$$\delta_{tot4} = \sqrt{\left(\frac{1}{R_1^2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^2} \cdot \delta_{R_1} \right)^2 + \left(\frac{1}{R_2^2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^2} \cdot \delta_{R_2} \right)^2 + \left(\frac{1}{R_3^2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^2} \cdot \delta_{R_3} \right)^2 + \dots}$$

$$+ \left(\frac{1}{R_4^2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^2} \cdot \delta_{R_4} \right)^2 = 0.0264$$

Exponential Sens Error ($R = \frac{V}{I}$)

$$\delta_R = \sqrt{\left(\frac{\delta_V}{I} \right)^2 + \left(\frac{\delta_I \cdot V}{I^2} \right)^2}$$

where $\begin{cases} R_1 = 99.0 \\ R_2 = 99.2 \\ R_3 = 980 \\ R_4 = 98.4 \end{cases}$ and $\begin{cases} \delta_{R_1} = 0.1 \\ \delta_{R_2} = 0.1 \\ \delta_{R_3} = 10 \\ \delta_{R_4} = 0.1 \end{cases}$

(Derived on Previous Page)

$R_1: 2.56 \pm 0.01$	} $V \pm \delta_V$	0.0260 ± 0.0001	} $I \pm \delta_I$
$R_2: 2.40 \pm 0.01$		0.0240 ± 0.0001	
$R_3: 2.5 \pm 0.1$		0.0511 ± 0.0001	
$R_4: 2.3 \pm 0.1$		0.0908 ± 0.0001	

$\{ \delta_V \}$ $\{ \delta_I \}$

→ Calculations

$$\delta_{R_1} = \sqrt{\left(\frac{0.01}{0.0260} \right)^2 + \left(\frac{0.0001 \cdot 2.56}{0.0260^2} \right)^2} = 0.5398 = 0.54$$


$$\delta_{R_2} = \sqrt{\left(\frac{0.01}{0.0240} \right)^2 + \left(\frac{0.0001 \cdot 2.40}{0.0240^2} \right)^2} = 0.5893 = 0.59$$

$$\delta_{R_3} = \sqrt{\left(\frac{0.1}{0.0511} \right)^2 + \left(\frac{0.0001 \cdot 2.5}{0.0511^2} \right)^2} = 1.9593 = 1.96$$

$$\delta_{R_4} = \sqrt{\left(\frac{0.1}{0.0908} \right)^2 + \left(\frac{0.0001 \cdot 2.3}{0.0908^2} \right)^2} = 1.1017 = 1.10$$

Partial Derivatives
found using
wolfram calculator
with python

Trevor & Pratham - Ohm's Law in Action

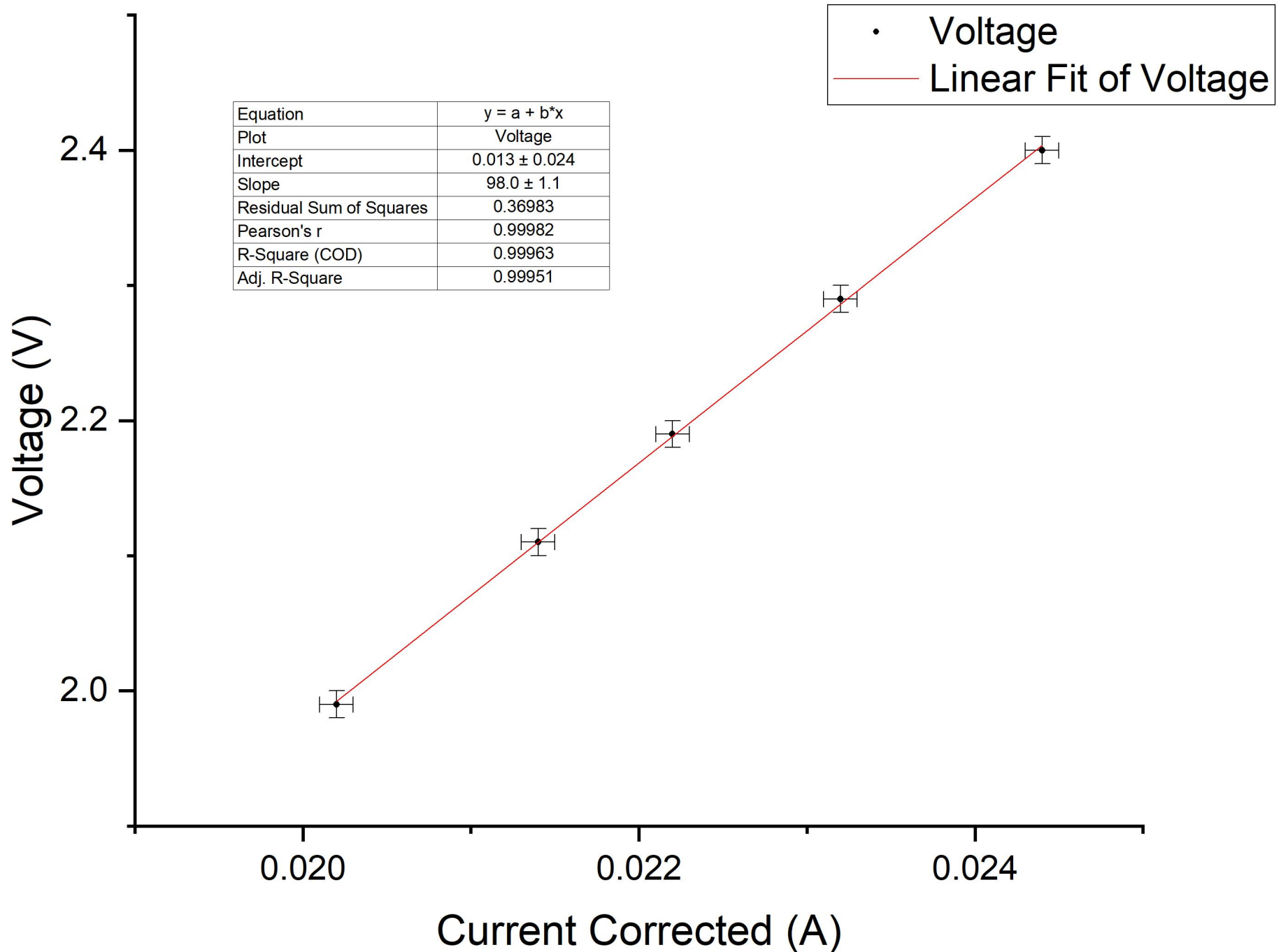

Trevor & Pratham - Ohm's Law Failure

