

☐ **PHYS115** ☐ **PHYS121** ☐ **PHYS123**  
☐ **PHYS116** ☒ **PHYS122** ☐ **PHYS124**  
**Lab Cover Letter**

Author (You) Trevor Swan Signature: Trevor Swan

*I declare that this assignment is original and has not been submitted for assessment elsewhere, and acknowledge that the assessor of this assignment may, for the purpose of assessing this assignment: (1) reproduce this assignment and provide a copy to another member of faculty; and/or (2) communicate a copy of this assignment to a plagiarism checking service (which may then retain a copy of this assignment on its database for the purpose of future plagiarism checking).*

Lab Partner(s) Pratham Bhashya Kurla

Date Performed 3/3/25 Date Submitted 3/18/25

Lab (such as #1: UNC) #4: RC-CIR

TA: Samantha

**GRADE** (to be filled in by your TA) See your TA for detailed feedback.  
 An 'x' next to a subcategory means you need to improve this aspect of your work.

**Paper Subtotals (points)**

- |  |   |
|--|---|
| <p>( ) <b>General (6)</b></p> <p>_____ Sig. figs.</p> <p>_____ Units</p> <p>_____ Clarity of Presentation</p> <p>_____ Format</p> <p>( ) <b>Abstract (4)</b></p> <p>_____ Quantity or principle</p> <p>_____ How measurement was made</p> <p>_____ Numerical Results</p> <p>_____ Conclusion</p> <p>( ) <b>Intro &amp; Theory (9)</b></p> <p>_____ Basic principle</p> <p>_____ Main equations to be used</p> <p>_____ Apparatus</p> <p>_____ What will be plotted</p> <p>_____ Fitting parameters related</p> <p>( ) <b>Exp. Procedures (15)</b></p> <p>_____ Description</p> <p>_____ Stating and justifying uncertainties</p> <p>_____ Data Record</p> <p>_____ Quality of Lab Work</p> <p>( ) <b>Analysis &amp; Error Analysis (20)</b></p> <p>_____ Discussion</p> <p>_____ Equations &amp; Calculations</p> <p>_____ Presentation inc. Graphs, Tables</p> <p>_____ Results Reported &amp; Reasonable</p> <p>_____ Underlined items addressed</p> | <p>( ) <b>Discussion &amp; Conclusions (6)</b></p> <p>_____ Numerical comparison of results</p> <p>_____ Logical conclusions</p> <p>_____ Discussion of pos. errors</p> <p>_____ Suggestions to reduce errors</p> <p>( ) <b>Paper Total (60 points)</b><br/> <b>(30 points for CME or EPF)</b></p> <p>( ) <b>Notebook (10 points)</b></p> <p>_____ Format (<i>proper style, following directions</i>)</p> <p>_____ Apparatus (<i>brief description of equipment, including sketches</i>)</p> <p>_____ Data (<i>including computer file names and manually recorded data</i>)</p> <p>_____ Experimental Technique (<i>describing your procedures; stating &amp; justifying uncerts.</i>)</p> <p>_____ Analysis (<i>results and errors</i>)</p> <p>( ) <b>Worksheet(s)/Fill-in-the-Blank-Report (30 points) if applicable</b></p> <p>( ) <b>Adjustments</b> – late submissions, improper procedures, etc. – or bonus points for exceptional work.</p> <p>( ) <b>Total Grade</b></p> <p>Graded by _____ (TA's initial)</p> |
|--|---|

# RC-CIR Worksheet

Your Name: Tavor Sun Signature: 

Lab partner(s): Pratham Bhashyakarla

Course & Section: 122-118 Station # B Date: 3/18/23

1. (Section E.2.) The nominal values of the resistance and capacitance are 10 kΩ and 47 μF, respectively. What are your measured values?

$R = \underline{10.31} \pm \underline{0.01} \underline{\text{ k}\Omega}$  (units)

$C = \underline{44.3} \pm \underline{0.1} \underline{\text{ }\mu\text{F}}$  (units)

2. (Section E.2.) What is the value of the time constant based on the measured values and nominal (labeled) values?

$\tau_{\text{measured}} = \underline{0.457} \underline{\text{ ms}}$  (units)

$\text{k}\Omega = \Omega \times 10^3$   
 $\mu\text{F} = \text{F} \times 10^{-6}$  }  $\Omega \text{ F} \times 10^{-3} = \text{s} \times 10^{-3}$

$\tau_{\text{labeled}} = \underline{0.470} \pm \underline{0.02} \underline{\text{ ms}}$  (units)

3. (Section E.7.) What is the maximum amount of charge stored on the capacitor during charging?

$Q = \underline{132.9} \pm \underline{0.1} \underline{\text{ }\mu\text{C}}$  (units)

$44.3 \mu\text{F} \times 3\text{V} = 132.9 \mu\text{C}$   
 $\delta_2 = \sqrt{0.1^2 + 0.1^2} = 0.14$

Note that you have taken two pairs of data sets, two while charging the capacitor and two while discharging it. From those graphs, read off the voltage across the resistor and the voltage across the capacitor at the end of each run.

*Charging*

$V_R = \underline{0} \pm \underline{0.1} \underline{\checkmark}$  (units)

$V_C = \underline{2.5} \pm \underline{0.1} \underline{\checkmark}$  (units)

*Discharging*

$V_R = \underline{0} \pm \underline{0.1} \underline{\checkmark}$  (units)

$V_C = \underline{2.1} \pm \underline{0.1} \underline{\checkmark}$  (units)

4. (Section E.7.) What should the two pairs of voltages add up to? Do they? Why or why not?

They should add to the power supply output value of 3V. This is due to Kirchhoff's Loop Rule,  $V_R + V_C = V_0 = 3\text{V}$ .

Charging $V_0 = 2.5\text{V}$	Discharging $V_0 = 2.1\text{V}$
---------------------------------	------------------------------------

These numbers are not consistent with the predicted 3V, indicates battery decay.

5. (Section G) What are the five values of the time constant?

$$\tau_{\text{measured}} = 0.4570 \pm 0.0001 \text{ s (units)} \quad \delta_{\tau} = \sqrt{0.1^2 + 0.01^2} = 0.1 \text{ ms} = 0.0001 \text{ s}$$

$$\tau_{\text{charging}_C} = 0.4735 \pm 0.0005 \text{ s (units)}$$

$$\tau_{\text{discharging}_C} = 0.4745 \pm 0.0005 \text{ s (units)}$$

$$\tau_{\text{charging}_R} = 0.4755 \pm 0.0006 \text{ s (units)}$$

$$\tau_{\text{discharging}_R} = 0.4737 \pm 0.0005 \text{ s (units)}$$

Compare these five values of the time constant to each other and discuss whether or not they are in agreement, within estimated errors.

Calc. total from 4 non-measured values

$$\tau_{\text{mean}} = 0.4743 \text{ s (units)} \quad \frac{0.4735 + 0.4745 + 0.4755 + 0.4737}{4} = 0.4743$$

$$\tau_{\text{std dev}} = 0.0009 \text{ s (units)} \quad \sqrt{\frac{(0.4735 - 0.4743)^2 + (0.4745 - 0.4743)^2 + (0.4755 - 0.4743)^2 + (0.4737 - 0.4743)^2}{4 - 1}} = 9 \times 10^{-4} \text{ s}$$


All  $\tau$  values except the measured & charging R values agree within four errors. These values are also captured by the mean  $\pm$  std dev  $\tau$  value. Ultimately, the five values are not in agreement!

$$\text{Therefore, } \tau = 0.4743 \pm 0.0009 \text{ s (units)}$$

6. (Section G) Does the residual plot indicate you had a good fit or a bad fit? Explain.

Not necessarily...

- Non-random pattern: There seems to be a wave-like pattern, not appearing randomly scattered around 0. This suggests systematic deviation from the model.

To be a good fit for the model, the residuals should mostly be near zero and should be randomly distributed with no obvious trends with the points and the error bars pointing to a sinusoidal pattern. This indicates that our model is not necessarily a good fit for the data. Roughly, the Residuals paint a shape close to: , which is not random (3/4 of fit is not).

7. (Section H) What are your measured values of the resistance and capacitance of the two capacitors?

$$R = 10.31 \pm 0.01 \text{ k}\Omega \text{ (units)}$$

$$C_1 = 44.3 \pm 0.1 \text{ }\mu\text{F} \text{ (units)}$$

$$C_2 = 44.0 \pm 0.1 \text{ }\mu\text{F} \text{ (units)}$$

8. (Section H) What is your calculated time constant for parallel capacitors? For series capacitors?

$$\tau_{\text{calc\_parallel}} = \underline{0.4104} \pm \underline{0.0001} \text{ s (units)}$$

$C_{\text{eq}} = C_1 + C_2 = 44.3 + 44.0 = 88.3 \mu\text{F}$

$$\delta_c = \sqrt{0.1^2 + 0.1^2} = 0.1 \quad \delta_{\tau} = \sqrt{0.14^2 + 0.01^2} = 0.14 \text{ ms}$$

$$\tau_{\text{calc\_series}} = \underline{0.22734} \pm \underline{0.00001} \text{ s (units)}$$

$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{44.3} + \frac{1}{44.0} \Rightarrow C_{\text{eq}} = 22.07 \mu\text{F}$

$$\delta_{c_1} = \left(\frac{1}{C_1^2}\right) \delta_{c_1} = \frac{1}{44.3^2} (0.1) = 5.1 \times 10^{-5} \text{ s} \quad \delta_{c_2} = \left(\frac{1}{C_2^2}\right) \delta_{c_2} = \frac{1}{44.0^2} (0.1) = 5.2 \times 10^{-5} \text{ s}$$

$$\delta_{\tau} = \sqrt{(5.1 \times 10^{-5})^2 + (5.2 \times 10^{-5})^2} = 7.3 \times 10^{-5} \text{ s}$$

9. (Section H) What is the time constant from the fit for parallel capacitors? For series capacitors?

$$\tau_{\text{fit\_parallel}} = \underline{0.441} \pm \underline{0.001} \text{ s (units)}$$

$$\tau_{\text{fit\_series}} = \underline{0.2393} \pm \underline{0.0005} \text{ s (units)}$$


10. (Section I) What are your measured values of the resistance and capacitance? What is the theoretical time constant?

$$R = \underline{1.00} \pm \underline{0.01} \text{ k}\Omega \text{ (units)}$$


$$C = \underline{0.455} \pm \underline{0.001} \text{ }\mu\text{F} \text{ (units)}$$

$$\tau = \underline{0.46} \pm \underline{0.01} \text{ ms (units)} \quad \delta_{\tau} = \sqrt{0.01^2 + 0.01^2} = 0.01 \text{ ms}$$

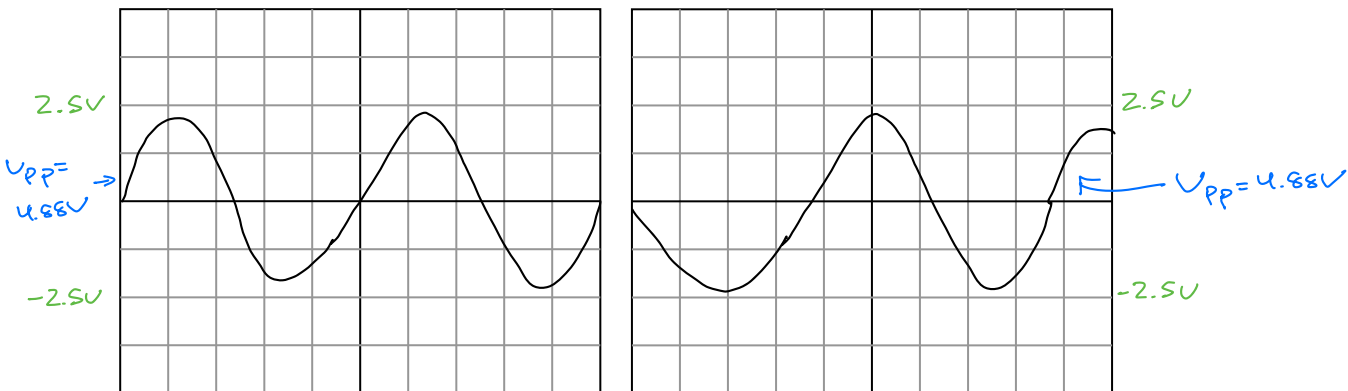
11. (Section I-analog differentiator) Sketch the waveforms you see for the sine wave and its derivative.



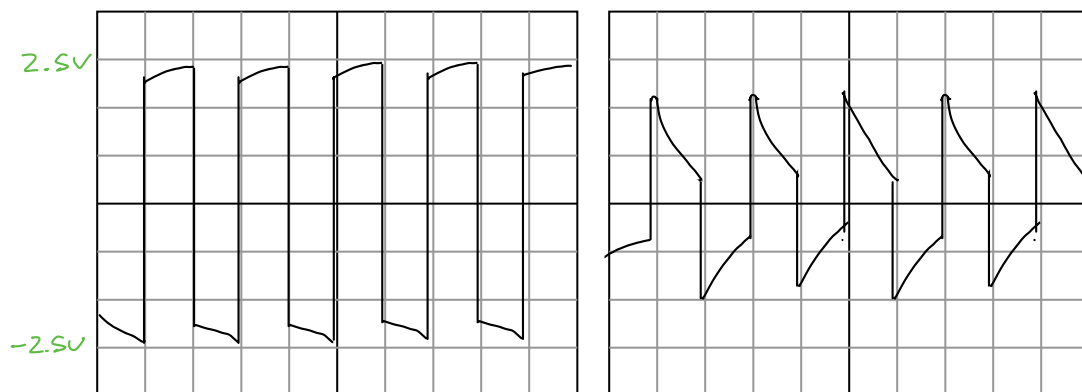12. (Section I-analog differentiator) Sketch the waveforms you see for the triangle wave and its derivative.



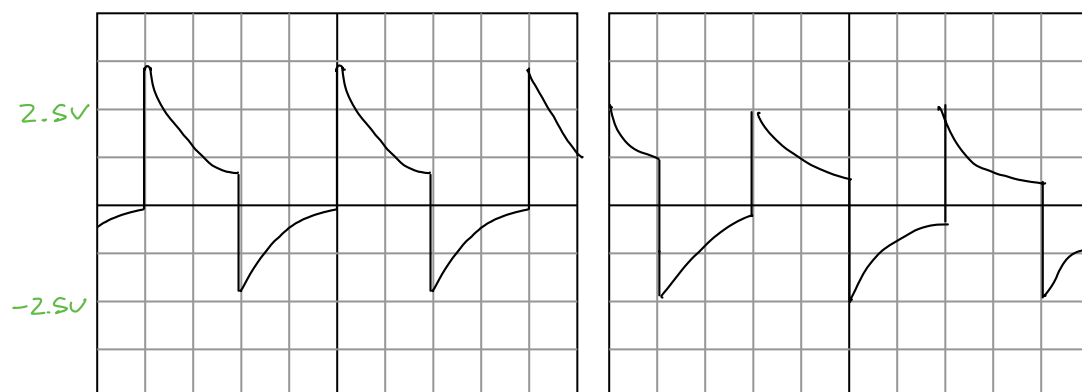
13. (Section I-analog differentiator) Sketch the waveforms you see for the square wave and its derivative.



**GRADE:** \_\_\_\_\_  
(out of 30 points)

**GRADED BY** \_\_\_\_\_  
(TA's initials)

Charging Capacitor

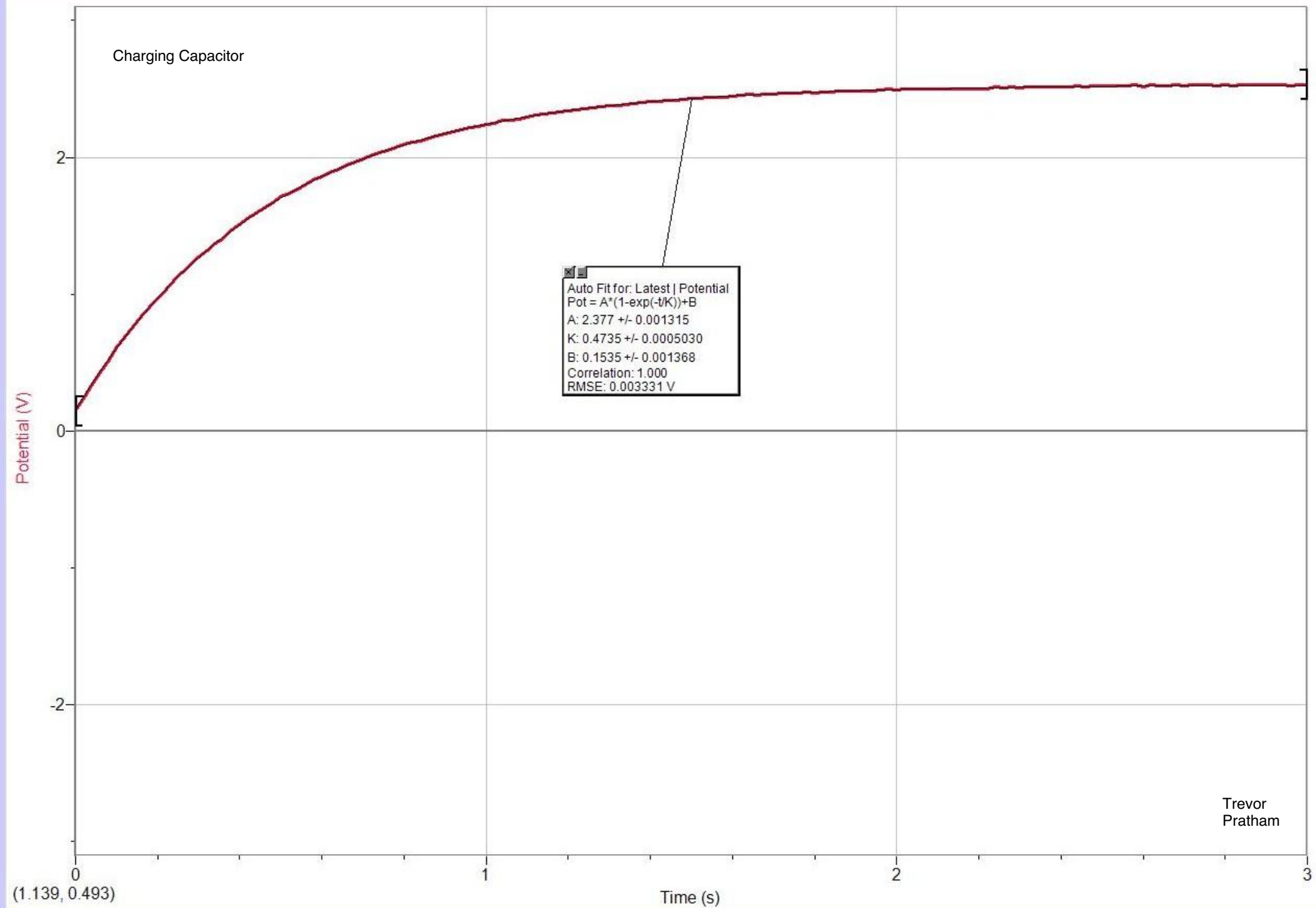

Charging Resistor

Auto Fit for: Latest | Potential  
Pot =  $A \cdot (1 - \exp(-t/K)) + B$   
A: 1.648 +/- 0.001141  
K: 0.4755 +/- 0.0006336  
B: -1.662 +/- 0.001188  
Correlation: 1.000  
RMSE: 0.002898 V

Potential (V)

(1.253, 0.813)

Time (s)

Trevor  
Pratham

Discharging Capacitor

2

0

-2


Auto Fit for: Latest | Potential  
Pot =  $A \cdot (1 - \exp(-t/K)) + B$   
A: -2.099 +/- 0.001227  
K: 0.4745 +/- 0.0005334  
B: 2.092 +/- 0.001277  
Correlation: 1.000  
RMSE: 0.003113 V

Trevor  
Pratham


Time (s)

(1.243, 0.843)



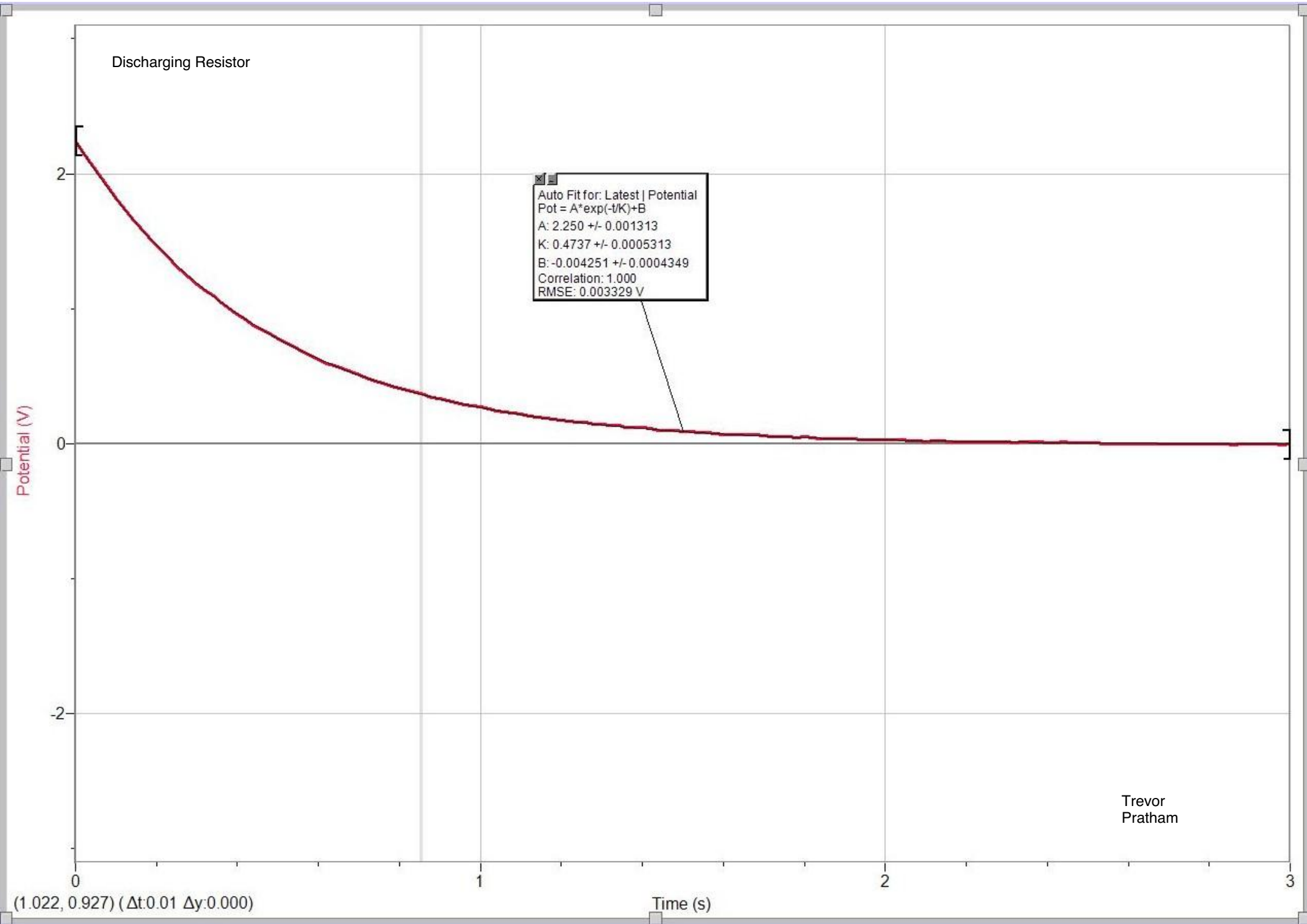


# Parallel Capacitor Charging

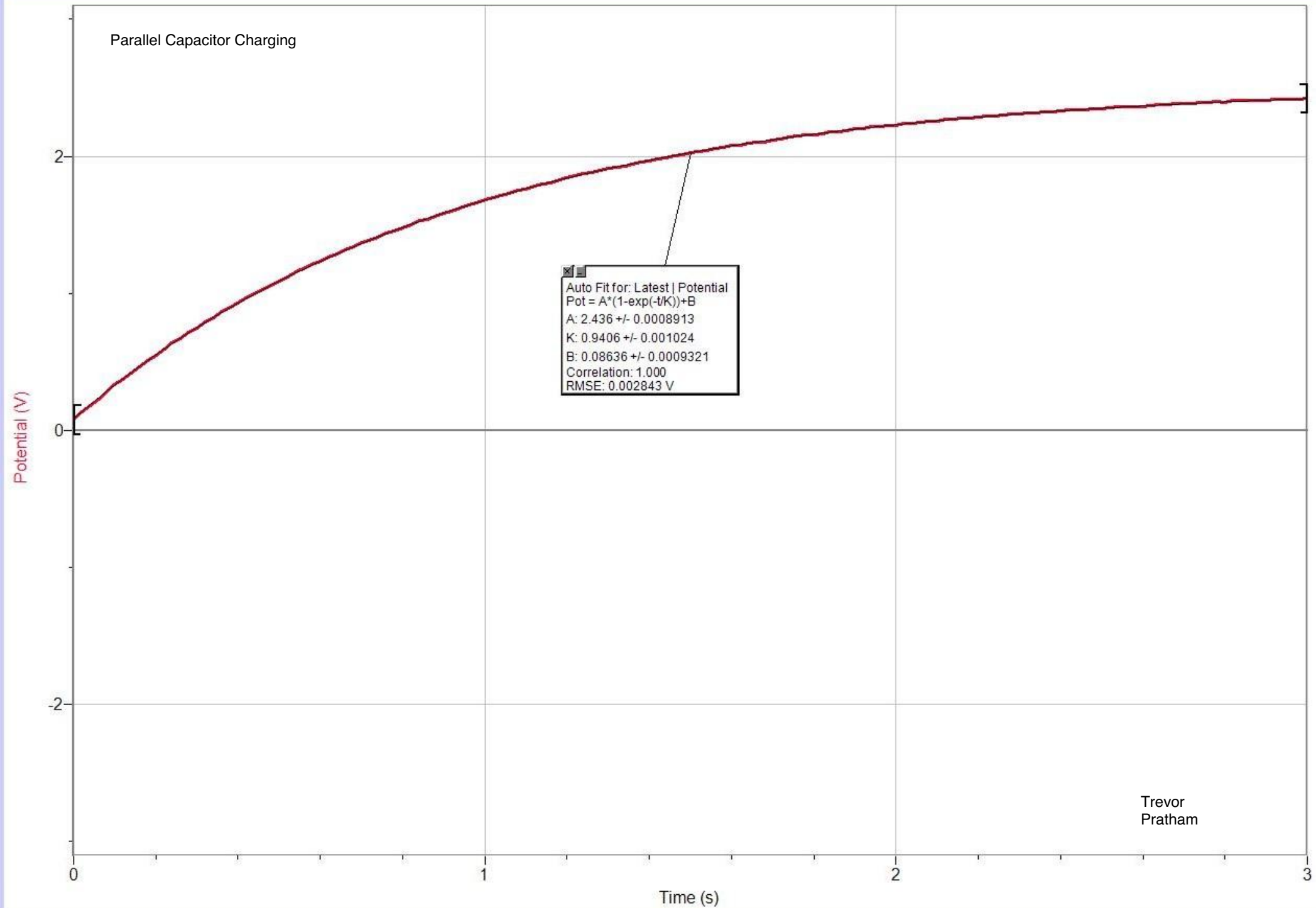


Trevor  
Pratham

# Series Capacitor Charging

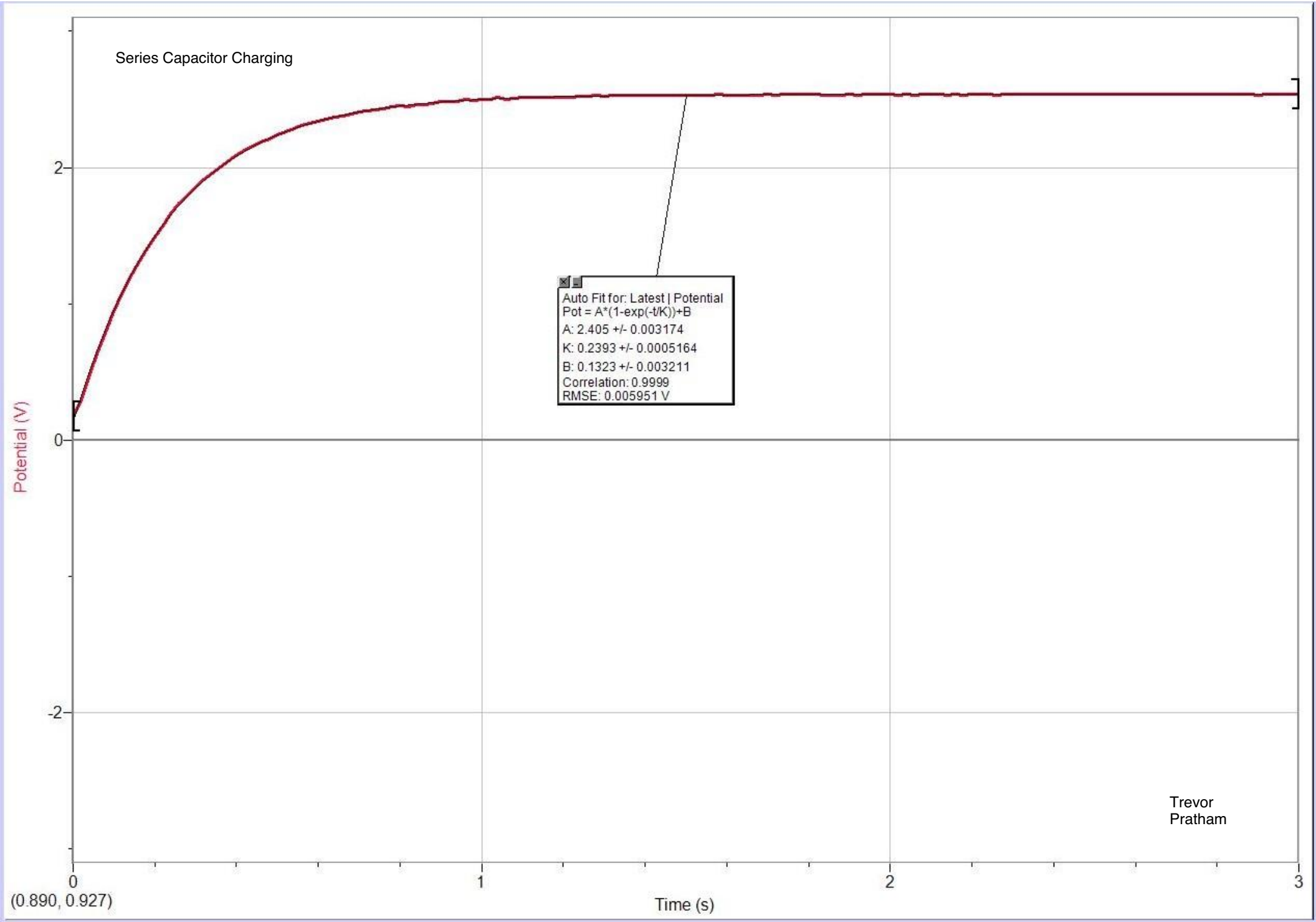

Trevor  
Pratham

# Charging Data for Capacitor

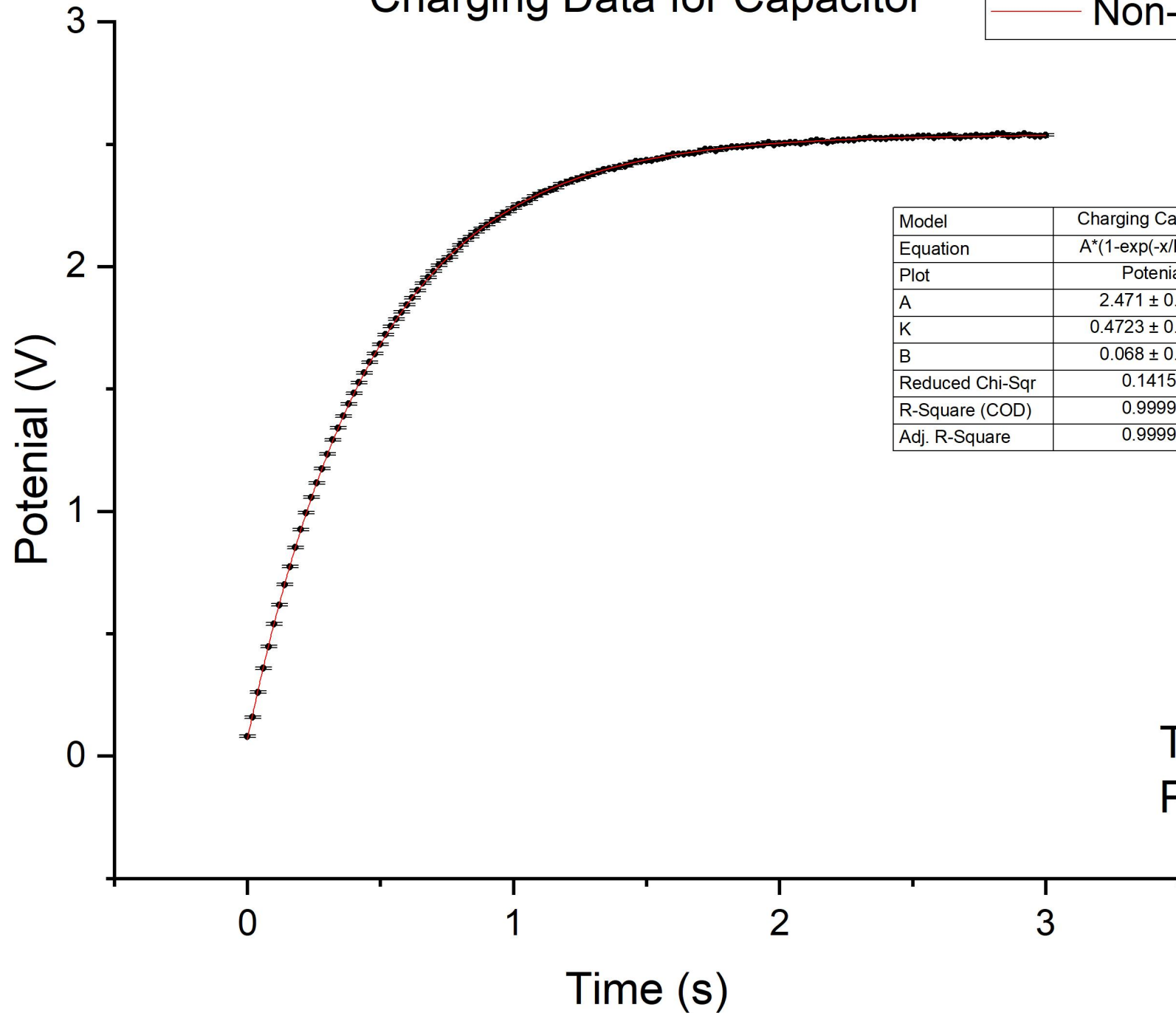


- Potenial
- Non-Linear Fit

Model	Charging Capacitor
Equation	$A*(1-\exp(-x/K)) + B$
Plot	Potenial
A	$2.471 \pm 0.001$
K	$0.4723 \pm 0.0005$
B	$0.068 \pm 0.002$
Reduced Chi-Sqr	0.14156
R-Square (COD)	0.99996
Adj. R-Square	0.99996

Trevor  
Pratham

# Residuals of Charged Capacitor Fit

• Residuals

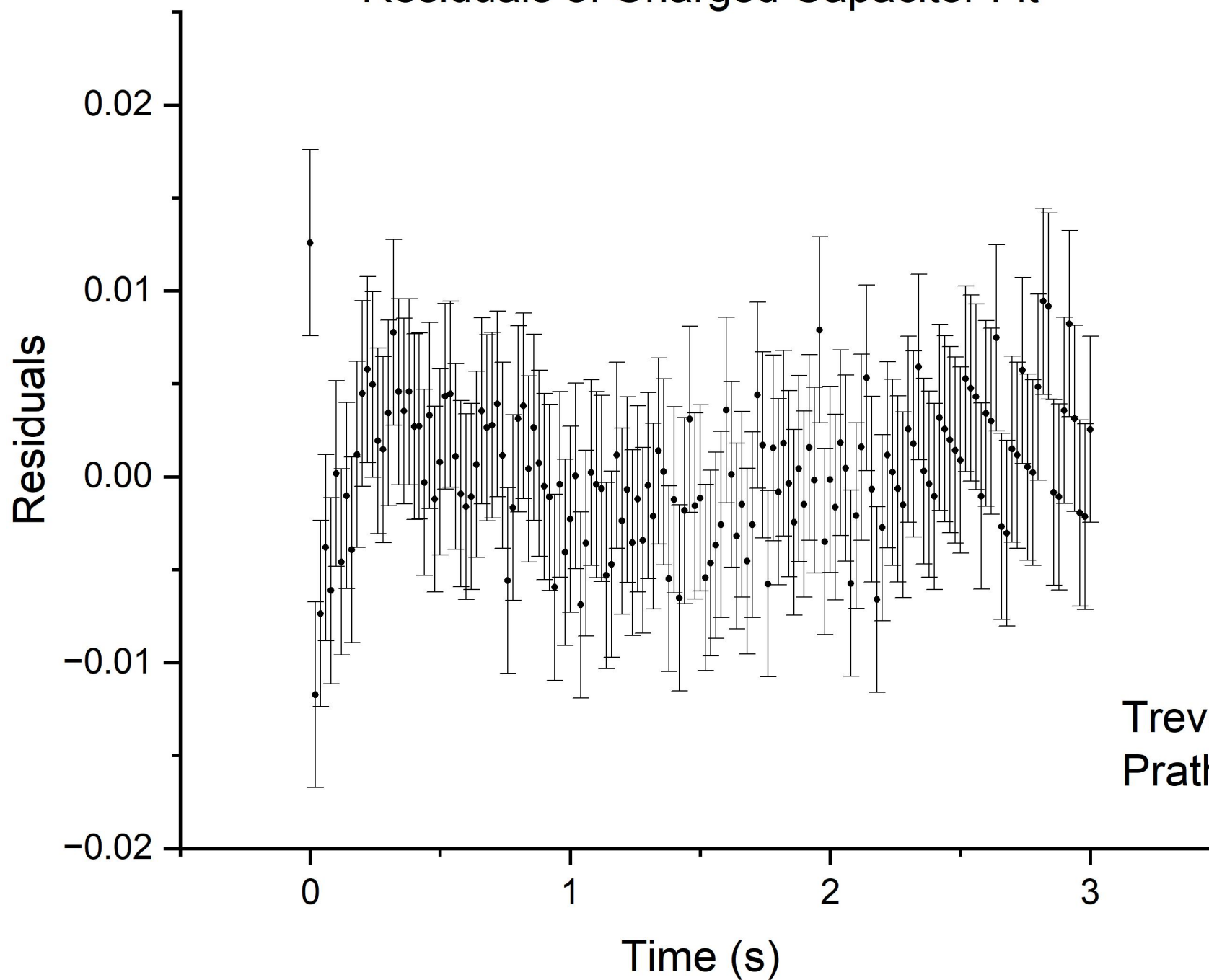

Trevor  
Pratham

