

RC-CIR Worksheet

Your Name: _____ Signature: _____

Lab partner(s): _____

Course & Section: _____ Station # _____ Date: _____

1. (Section E.2.) The nominal values of the resistance and capacitance are $10\text{ k}\Omega$ and $47\text{ }\mu\text{F}$, respectively. What are your measured values?

$R = \text{_____} \pm \text{_____}$ (units)

$C = \text{_____} \pm \text{_____}$ (units)

2. (Section E.2.) What is the value of the time constant based on the measured values and nominal (labeled) values?

$\tau_{\text{measured}} = \text{_____}$ (units)

$\tau_{\text{labeled}} = \text{_____} \pm \text{_____}$ (units)

3. (Section E.7.) What is the maximum amount of charge stored on the capacitor during charging?

$Q = \text{_____} \pm \text{_____}$ (units)

Note that you have taken two pairs of data sets, two while charging the capacitor and two while discharging it. From those graphs, read off the voltage across the resistor and the voltage across the capacitor at the end of each run.

Charging

$V_R = \text{_____} \pm \text{_____}$ (units)

$V_C = \text{_____} \pm \text{_____}$ (units)

Discharging

$V_R = \text{_____} \pm \text{_____}$ (units)

$V_C = \text{_____} \pm \text{_____}$ (units)

4. (Section E.7.) What should the two pairs of voltages add up to? Do they? Why or why not?

5. (Section G) What are the five values of the time constant?

$$\tau_{\text{measured}} = \text{_____} \pm \text{_____} \text{ (units)}$$

$$\tau_{\text{charging_C}} = \text{_____} \pm \text{_____} \text{ (units)}$$

$$\tau_{\text{discharging_C}} = \text{_____} \pm \text{_____} \text{ (units)}$$

$$\tau_{\text{charging_R}} = \text{_____} \pm \text{_____} \text{ (units)}$$

$$\tau_{\text{discharging_R}} = \text{_____} \pm \text{_____} \text{ (units)}$$

Compare these five values of the time constant to each other and discuss whether or not they are in agreement, within estimated errors.

$$\tau_{\text{mean}} = \text{_____} \text{ (units)}$$

$$\tau_{\text{std dev}} = \text{_____} \text{ (units)}$$

$$\text{Therefore, } \tau = \text{_____} \pm \text{_____} \text{ (units)}$$

6. (Section G) Does the residual plot indicate you had a good fit or a bad fit? Explain.

7. (Section H) What are your measured values of the resistance and capacitance of the two capacitors?

$$R = \text{_____} \pm \text{_____} \text{ (units)}$$

$$C_1 = \text{_____} \pm \text{_____} \text{ (units)}$$

$$C_2 = \text{_____} \pm \text{_____} \text{ (units)}$$

8. (Section H) What is your calculated time constant for parallel capacitors? For series capacitors?

$\tau_{\text{calc_parallel}} = \text{_____} \pm \text{_____} \text{ (units)}$

$\tau_{\text{calc_series}} = \text{_____} \pm \text{_____} \text{ (units)}$

9. (Section H) What is the time constant from the fit for parallel capacitors? For series capacitors?

$\tau_{\text{fit_parallel}} = \text{_____} \pm \text{_____} \text{ (units)}$

$\tau_{\text{fit_series}} = \text{_____} \pm \text{_____} \text{ (units)}$


10. (Section I) What are your measured values of the resistance and capacitance? What is the theoretical time constant?

$R = \text{_____} \pm \text{_____} \text{ (units)}$



$C = \text{_____} \pm \text{_____} \text{ (units)}$

$\tau = \text{_____} \pm \text{_____} \text{ (units)}$


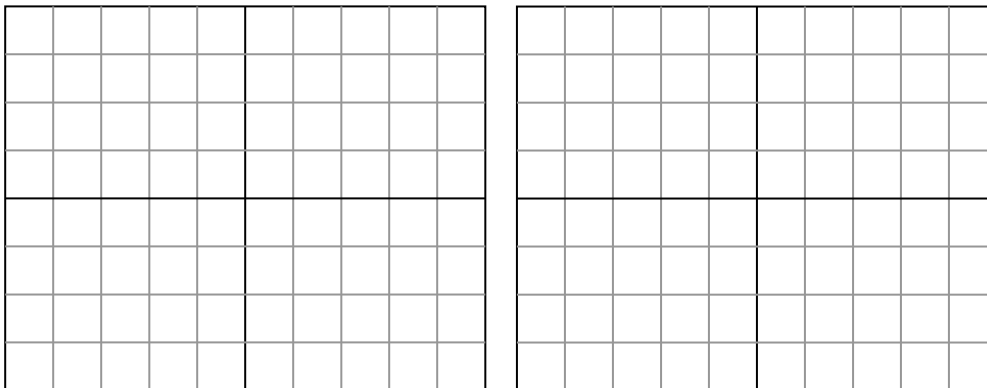
11. (Section I-analog differentiator) Sketch the waveforms you see for the sine wave and its derivative.



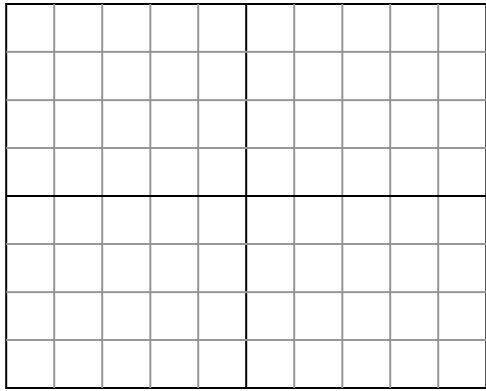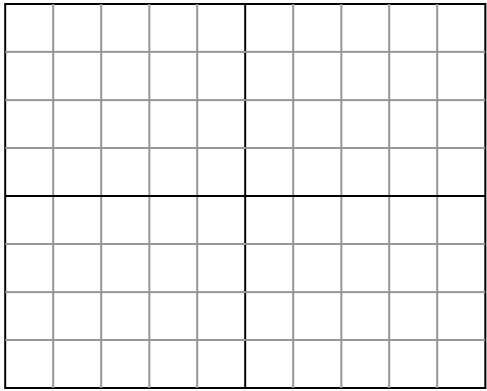12. (Section I-analog differentiator) Sketch the waveforms you see for the triangle wave and its derivative.



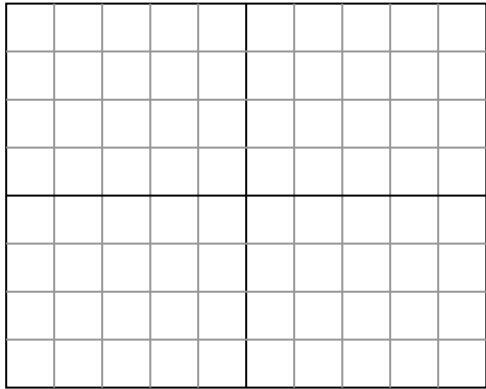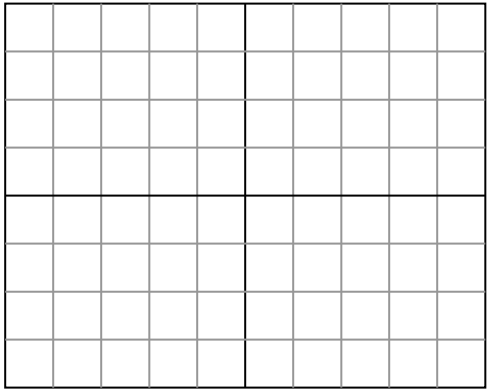13. (Section I-analog differentiator) Sketch the waveforms you see for the square wave and its derivative.



GRADE: _____
(out of 30 points)

GRADED BY _____
(TA's initials)